

Part 1: sizing chart

- 1) From the square law, we have

$$gm = \frac{2I_D}{V_{OV}} \rightarrow V_{OV} = \frac{2I_D}{gm}$$

For a real MOSFET, if we compute V_{OV} and $2 gm/ID$ they will not be equal. Let's define a new parameter called V-star (V^*) which is calculated from actual simulation data using the formula.

$$V^* = \frac{2I_D}{gm} \leftrightarrow gm = \frac{2I_D}{V^*}$$

The lower the V^* the higher the gm , but the larger the area and the lower the speed. An often-used sweet spot that provides good compromise between different trade-offs is $V^* = 200mV$.

- 2) Although the V^* is a nice parameter that is inspired by the square-law, it does not have an intuitive or a physical meaning (it is not an actual voltage in the circuit). We defined V^* to be able to define a relation between the gm and I_D . Thus, the real parameter that we should care about is the gm over I_D ratio (gm/ID).
- 3) There are many good things about using the gm/ID as a design knob:
- 4) a. The gm/ID gives a direct relation between the most important MOSFET parameter (gm) and the most valuable resource (ID). For example, a $gm/ID = 10 S/A$ means you get $10 \mu S$ of gm for every $1 \mu A$ of bias current.
- b. The gm/ID is a normalized knob: it has a limited search range (typically from 5 to 25 S/A) independent of the technology or the device type.
- c. The gm/ID is intuitive because it tells you directly about the inversion level (bias point) and consequently all related trade-offs. For example, $gm/ID = 5 S/A$ means strong inversion (SI), $gm/ID = 15 S/A$ means moderate inversion (MI), and $gm/ID = 25 S/A$ means weak inversion (WI).
- d. The gm/ID is an orthogonal knob: If we define the gm/ID then we define the inversion level (bias point). If you change ID or L while keeping gm/ID fixed, then the inversion level (bias point) is kept fixed. The W is treated as an output variable instead of being treated as an
- e. The higher the gm/ID (the lower the V^*) the higher the efficiency, but the larger the area and the lower the speed. An often-used sweet spot that provides good compromise between different trade-offs is $gm/ID = 10 S/A$ ($V^* = 200mV$).

Parameter	Value
$A_v = gm r_o^1$	50
gm/ID	$10 S/A$
Supply (V_{DD})	$1.8 V$
Quiescent (DC) output voltage	$V_{DD}/2 = 0.9 V$
Current consumption	$20 \mu A$

By using Sizing assistant, I have parameters $I_D = 20\mu A$ $\frac{gm}{I_D} = 10 S/A$

$$\frac{gm}{g_{ds}} = 50 \quad V_{DS} = 0.9V \quad V_{SB} = 0$$

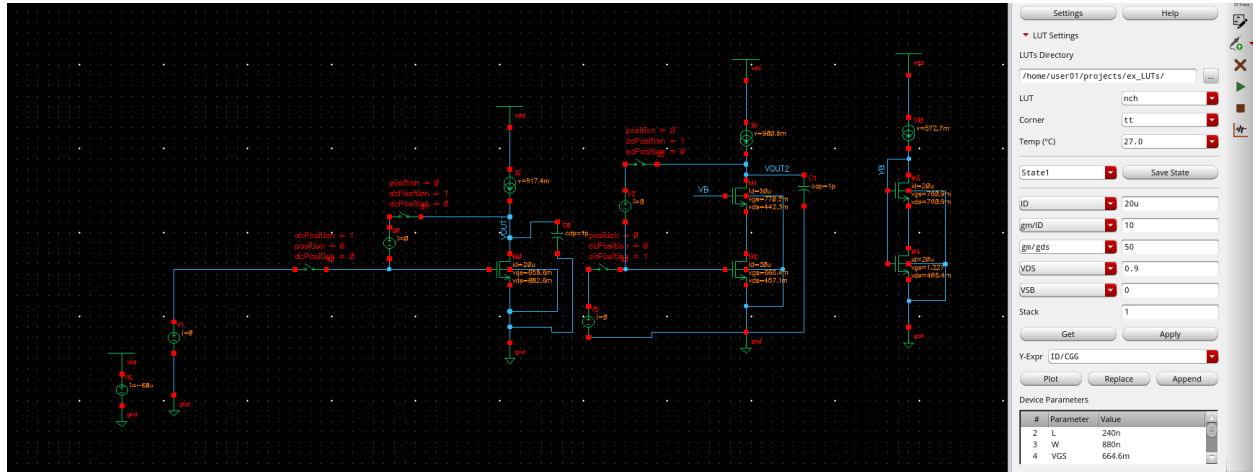


Figure 1 Sizing assistant results.

After using SA that generate the values of W,L and V_{GS}

$$W = 880nm \quad L = 240nm \quad V_{GS} = 664.6mV$$

Part 2: Cascode for Gain:

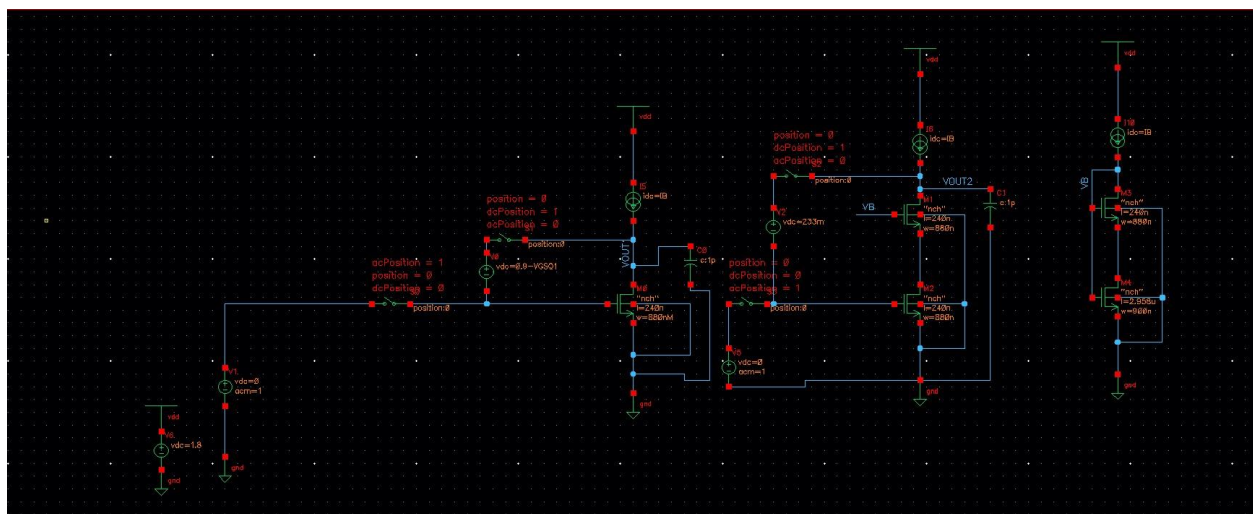


Figure 2 schematic

This parameter of schematic:

Use $I_B = 20\mu A$. Use L and W as selected in Part 1 for M0, M1, M2, and M4. Use the same W for M3 but it will have a different L as will be shown later. Use $C_L = 1pF$

In common source amplifier we have $V_{DS} = 0.9V$

In cascode amplifier we have for both transistor $V_{DS} = 0.45V$

but upper NMOS has v_{SB} not equal zero because source of this trans not connected to source, it has $V_{SB} = 0.45V$

$$V_B = V_{GS2} + V_{DS1}$$

Using sizing assistant to get this V_{GS2}

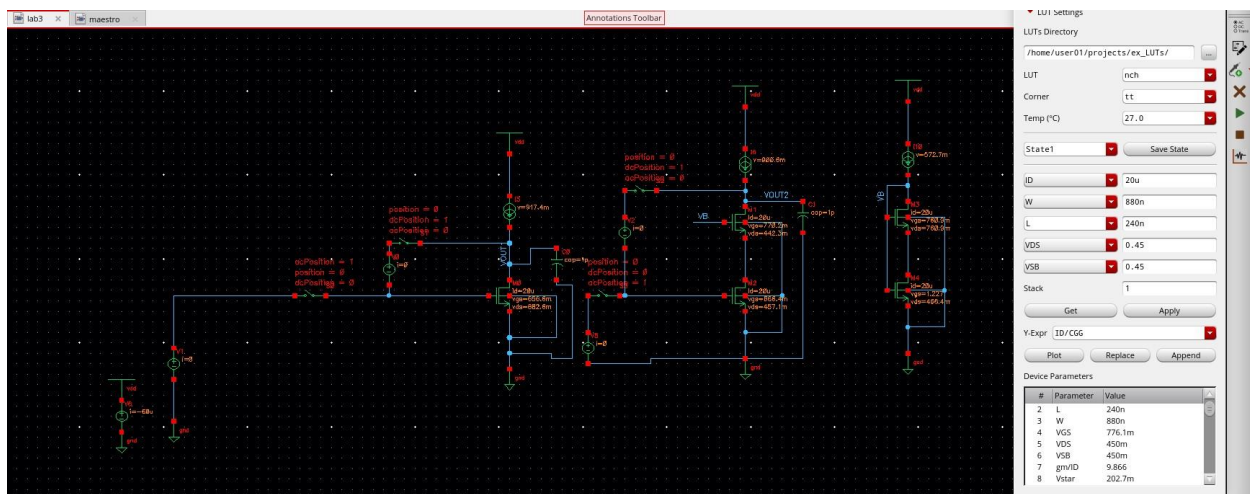


Figure 3 Sizing assistant of cascode amplifier

From SA we get $V_{GS2} = 776.1mV$ then

$$V_B = V_{GS2} + V_{DS1} = 0.45 + 0.776 = 1.226V$$

• M3 and M4 are used to generate the cascode bias voltage we want to get dimensions

Of M4 I want to get L and I have $V_B = V_{GS4,3} = 1.226V$

By plotting $V_{GS4,3}$ vs L using sizing assistant and trace L

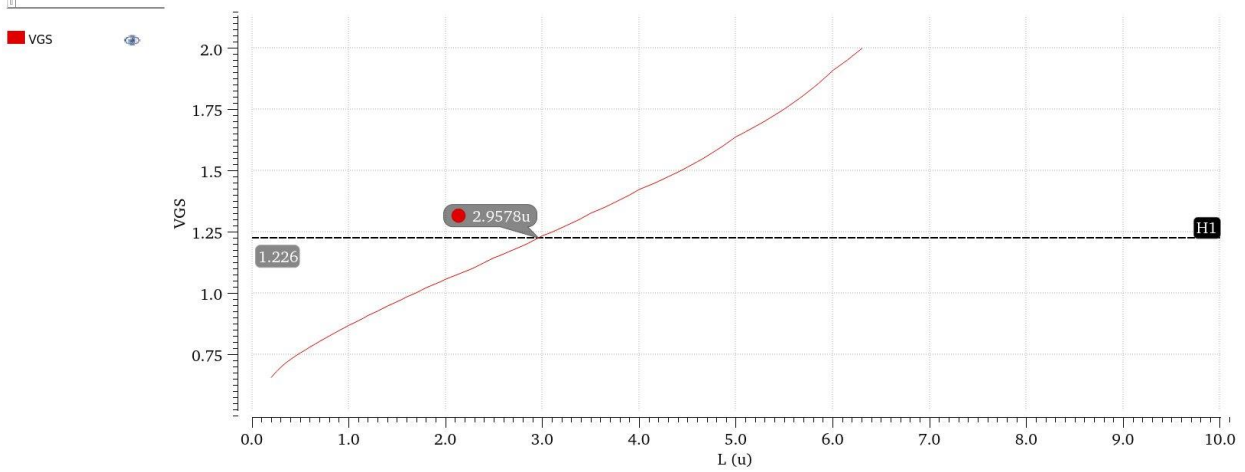


Figure 4 Trace to get L

After tracing $L=2.9578\mu\text{m}$

DC Analysis:

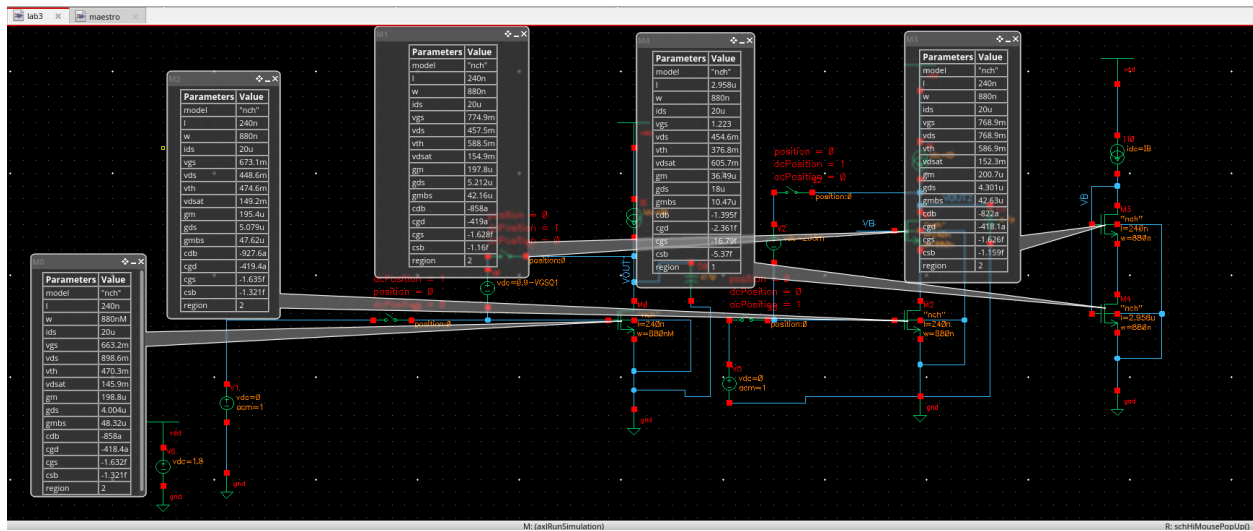


Figure 5 DC operating point

9) all transistors operate in saturation region except M4(in my schematic) operate in triode because

$$V_B = V_{GS} \quad V_B = V_{DS1} + V_{DS2}$$

Then $V_{GS} > V_{DS}$ then M4(in my schematic) is always in triode

10) All transistors don't have the same threshold voltage even they have the same channel length L , this due to body effect we notice that M0 and M2 (in my schematic) have V_{TH} is almost the same, but M1 have different V_{TH} because of body effect as source and bulk are not connected to each other so we will have voltage V_{sb} between them which increase value of V_{TH} .

11) $g_m \gg g_{ds}$.

$g_m > g_{mb}$.

$C_{gs} > C_{gd}$.

$C_{sb} > C_{db}$.

2. AC Analysis

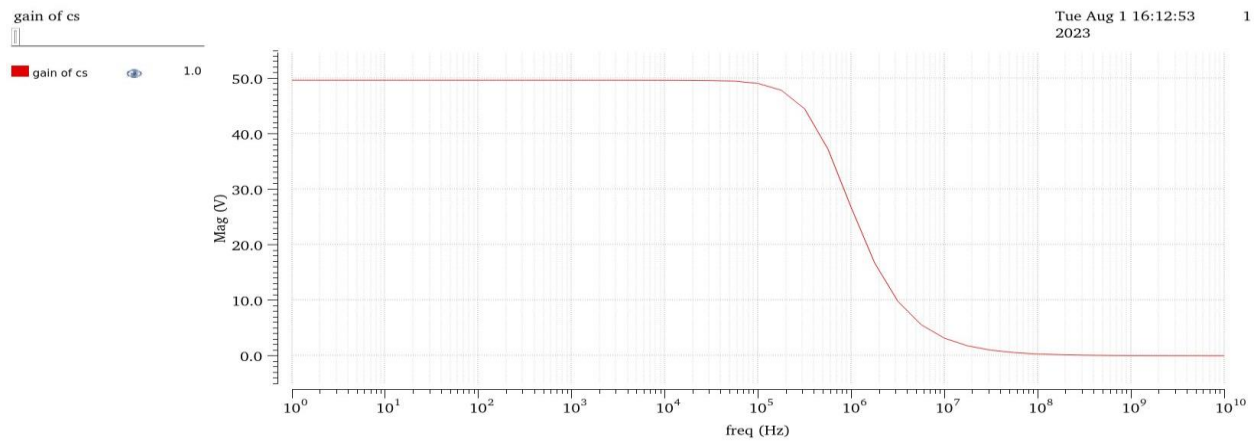


Figure 6 gain of common source

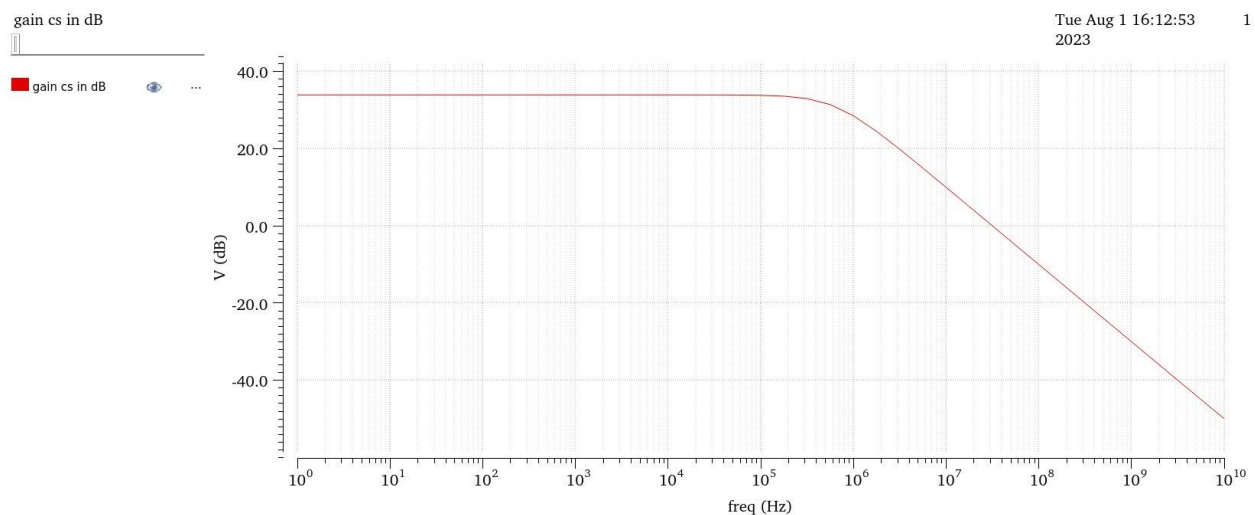


Figure 7 gain of common source in dB

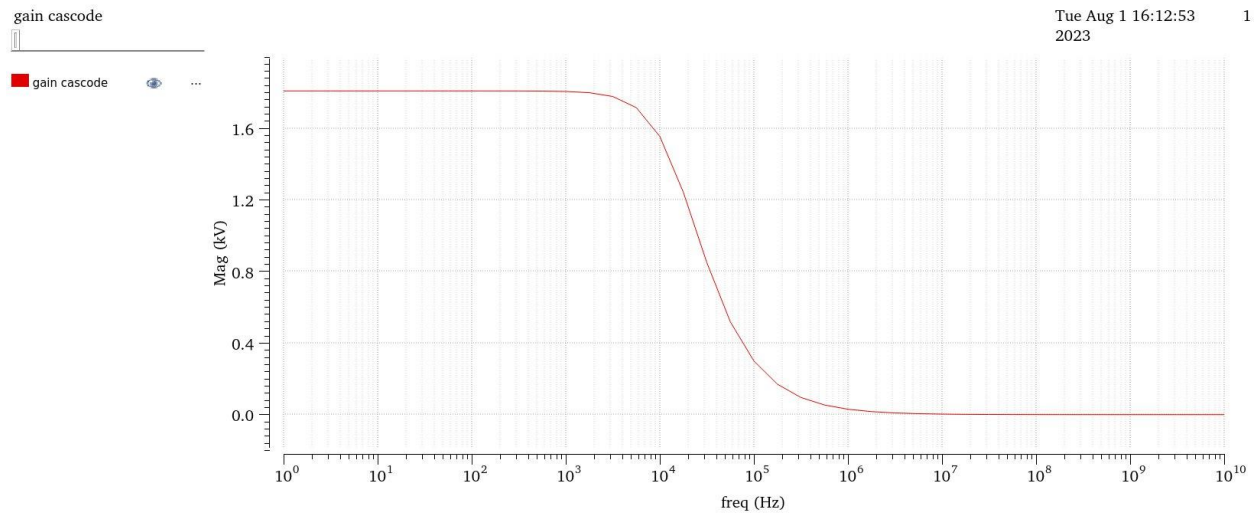


Figure 7 gain of cascode

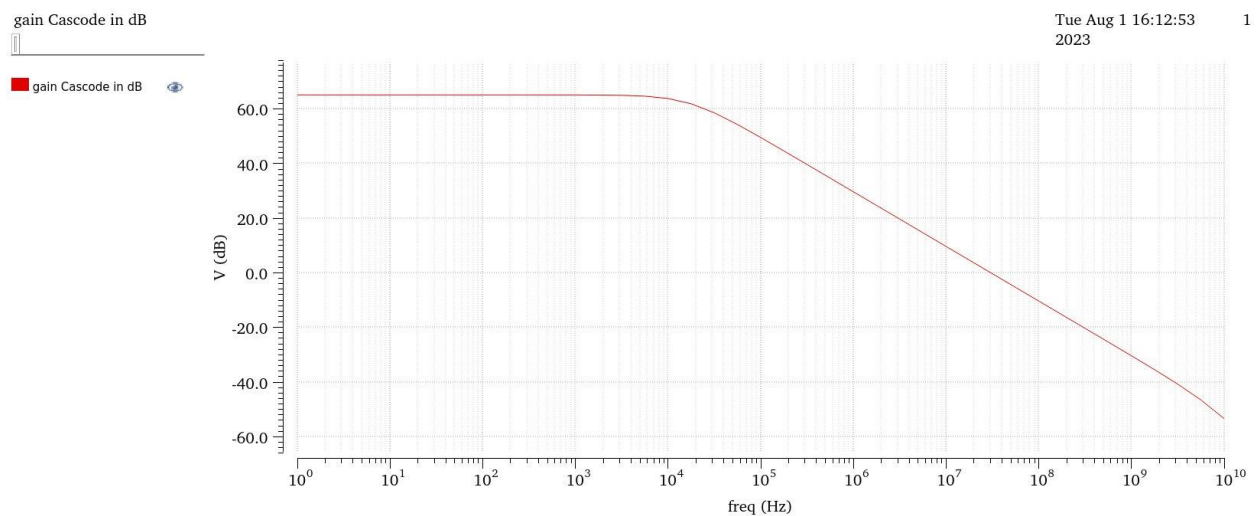


Figure 8 gain of cascode in dB

- from simulation we found:

$$A_{vcs} = 49.65$$

$$A_{vcascode} = 1.809K$$

Comment: cascode amplifier gain is greater than common source amplifier gain.

gain Cascode in dB

Tue Aug 1 16:12:53
2023

1

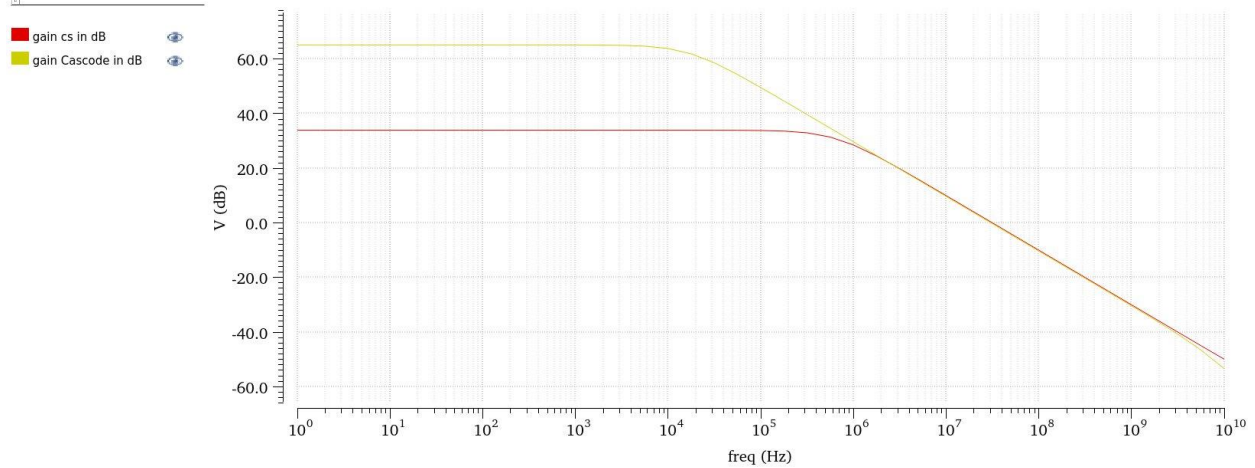


Figure 9 graph of cs and cascode bode plot on same graph

lab3_lab3_1	gain of cs				
lab3_lab3_1	gain cs in dB				
lab3_lab3_1	gain cascode				
lab3_lab3_1	gain Cascode in ...				
lab3_lab3_1	dc gain cs	49.65			
lab3_lab3_1	dc gain cs in dB	33.92			
lab3_lab3_1	dc gain cascode	1.809K			
lab3_lab3_1	dc gain cascode ...	65.15			
lab3_lab3_1	bandwidth cs	647.7K			
lab3_lab3_1	bandwidth casc...	16.84K			
lab3_lab3_1	gbw cs	32.24M			
lab3_lab3_1	gbw cascode	30.54M			
lab3_lab3_1	ugf cs	31.6M			
lab3_lab3_1	ugf cascode	30.92M			

Figure 10 results from adexl

RESULTS from ADEXL:

	Common source	Cascode amplifier
Gain	49.65	1.809K
Gain in dB	33.92	65.15
BW	647.7K	16.84K
GBW	32.24M	30.54M
UGF	31.6M	30.92M

Hand analysis:

$$|A_{VCS}| = g_{m1} * r_o = g_{m1} * \frac{1}{g_{ds}} = 198.8\mu * \frac{1}{4.004\mu} = 49.65$$

$$|A_{VCascode}| = g_{m1} * (r_{o1} + r_{o2} + (g_{m2} + g_{mb2}) * r_{o1} * r_{o2})$$

$$=195.4\mu * \left(\frac{1}{5.079\mu} + \frac{1}{5.212\mu} + (197.8\mu + 42.16\mu) * \frac{1}{5.079\mu} * \frac{1}{5.212\mu} \right) = 1.847K$$

$$BW_{CS} = \frac{1}{2\pi * R * C} = \frac{1}{2\pi * \frac{1}{4.004\mu} * 10^{-12}} = 637.256KHZ$$

$$BW_{Cascode} = \frac{1}{2\pi * R * C} = \frac{1}{2\pi * 9452.405 * 10^3 * 10^{-12}} = 16.838KHZ$$

$$GBW_{CS} = BW_{CS} * Gain_{CS} = 637.256K * 49.65 = 31.64MHZ$$

$$GBW_{Cascode} = BW_{cascode} * Gain_{Cascode} = 1.847K * 16.838K = 31.1MHZ$$

$$UGF \approx GBW$$

Comment:

As shown in previous results The cascode amplifier has a higher gain than the common source amplifier because the common base transistor in the cascode amplifier effectively multiplies the output resistance of the common source transistor. This is because the common base transistor has a very high output resistance, which is not affected by the input voltage because of higher resistance of cascode amplifier than common source, cascode has lower bandwidth as bandwidth.

	Simulator	Hand analysis
Gain CS	49.65	49.65
Gain Cascode	1.809K	1.847
BW CS	647.7K	637.256K
BW cascode	16.84K	16.838K
GBW CS	32.24M	31.64M
GBW Cascode	30.54M	31.1M
UGF CS	31.6M	31.64M
UGF Cascode	30.92M	31.1M

PART 3 [Optional]: Cascode for BW

1. OP Analysis

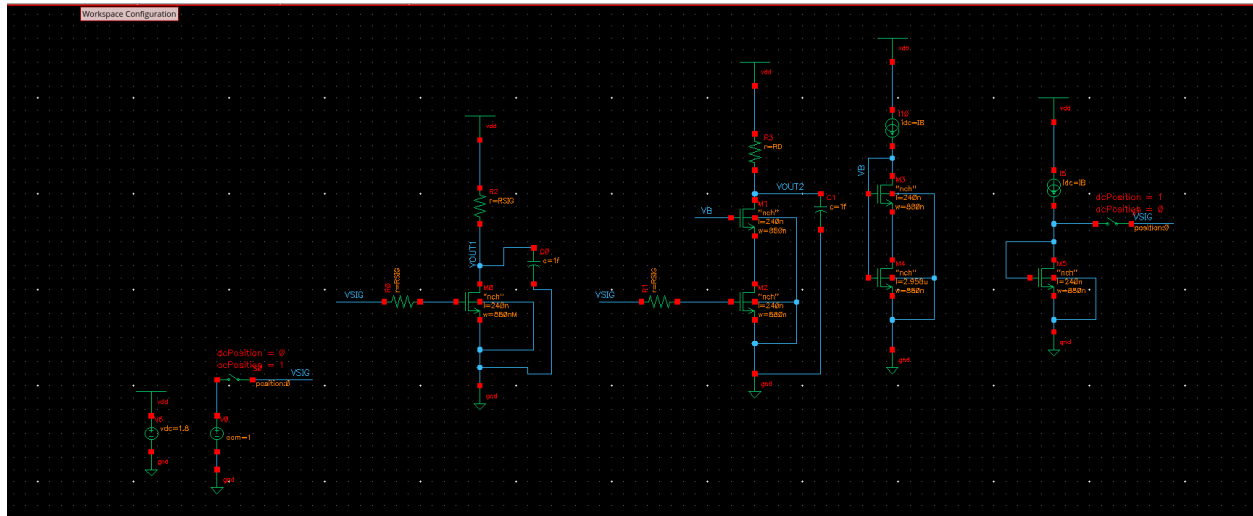


Figure 11 Schematic

$$2) RD = \frac{0.9}{20\mu} = 45K\Omega$$

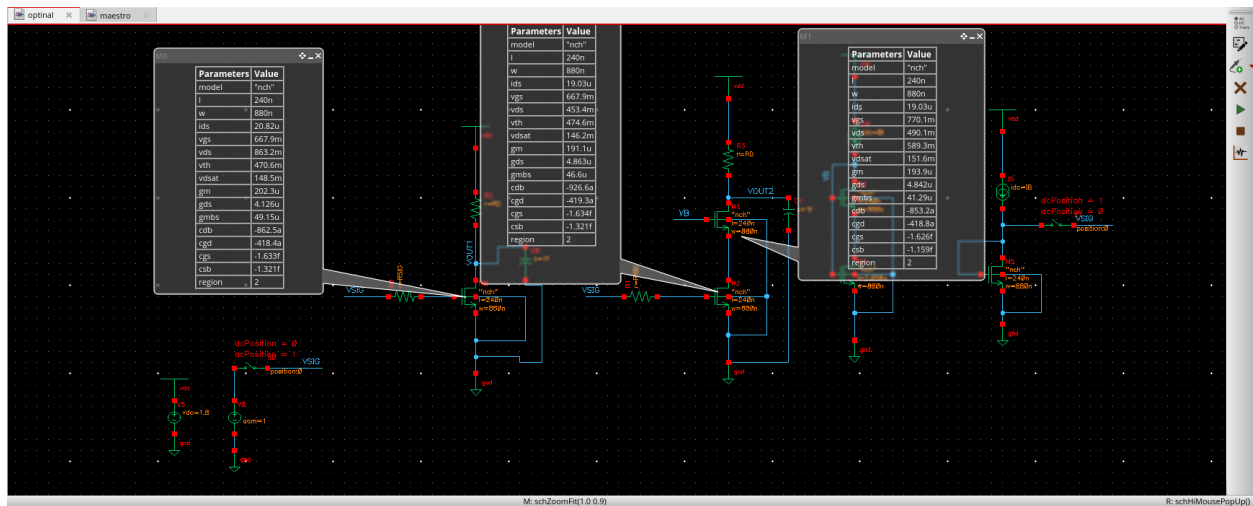


Figure 12 DC Operating point

3) as shown in figure all transistor operating in sat region (region 2).

2. AC Analysis

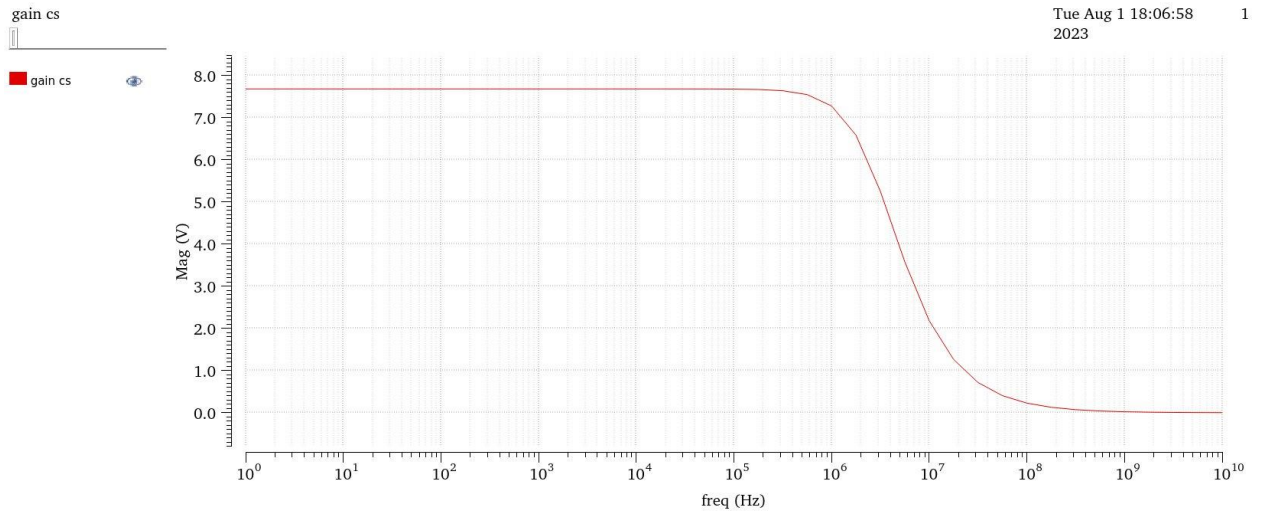


Figure 13 cs gain

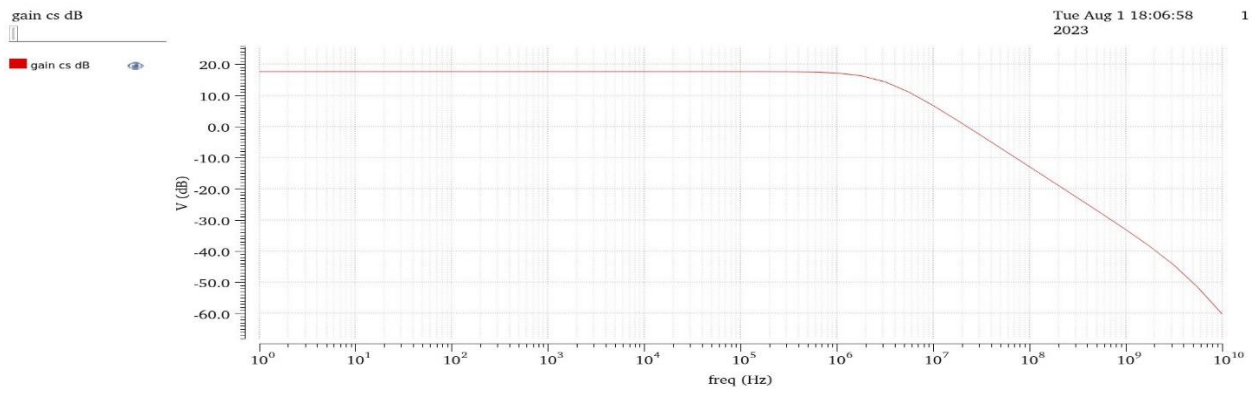


Figure 14 cs gain in dB

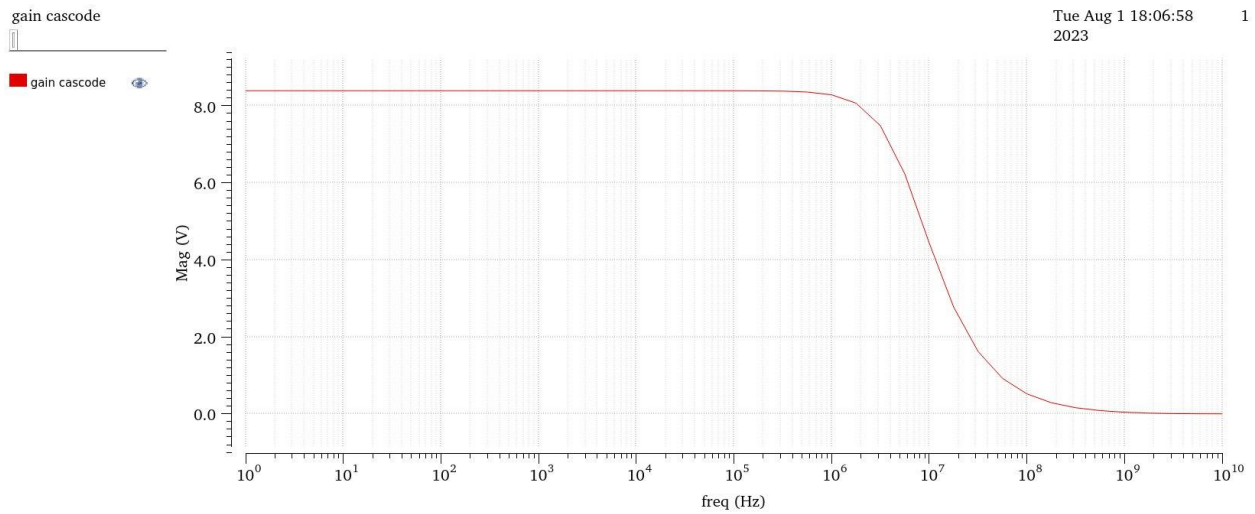


Figure 15 cascode gain

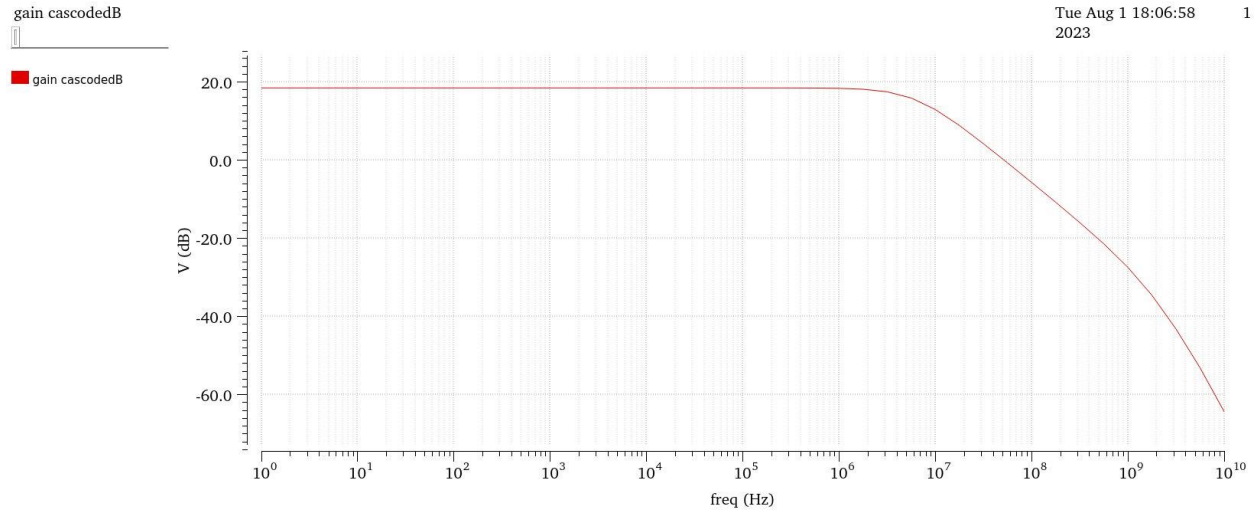


Figure 16 cascode gain in dB

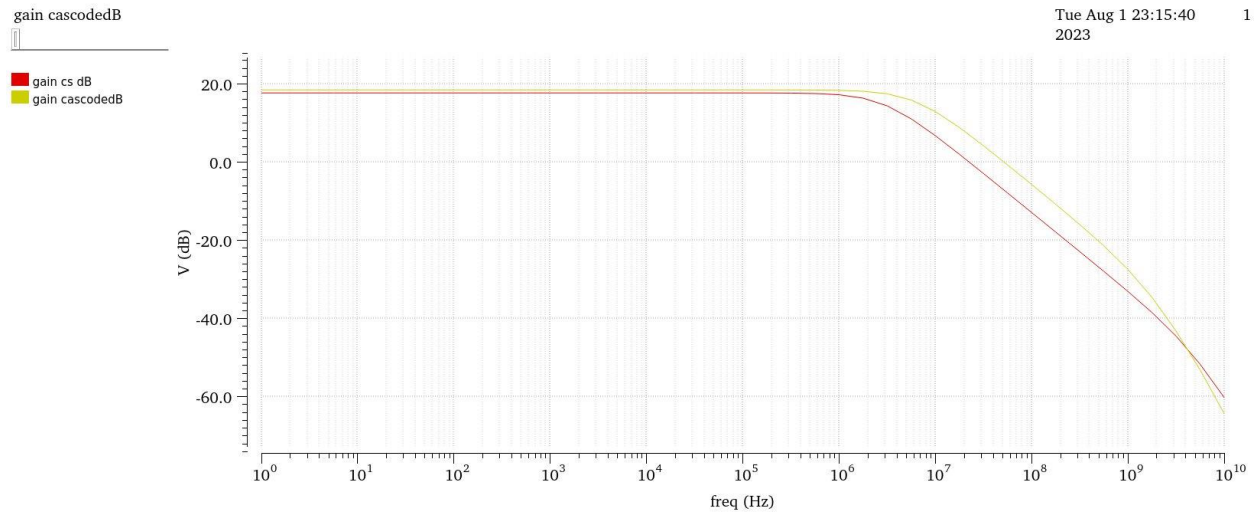


Figure 17 bode plot of cs and cascode

gain cs	expr	VR("/VOUT1")				<input checked="" type="checkbox"/>	<input type="checkbox"/>
gain cs dB	expr	dB20(VR("/VOUT1"))				<input checked="" type="checkbox"/>	<input type="checkbox"/>
gain cascode	expr	VR("/VOUT2")				<input checked="" type="checkbox"/>	<input type="checkbox"/>
gain cascodedB	expr	dB20(VR("/VOUT2"))				<input checked="" type="checkbox"/>	<input type="checkbox"/>
dc gain cs	expr	ymax(mag(VR("/VOUT1")))		7.678		<input checked="" type="checkbox"/>	<input type="checkbox"/>
dc gain cs dB	expr	ymax(dB20(VR("/VOUT1")))		17.71		<input checked="" type="checkbox"/>	<input type="checkbox"/>
dc gain cascode	expr	ymax(mag(VR("/VOUT2")))		8.391		<input checked="" type="checkbox"/>	<input type="checkbox"/>
dc gain cascode dB	expr	ymax(dB20(VR("/VOUT2")))		18.48		<input checked="" type="checkbox"/>	<input type="checkbox"/>
bandwidth cs	expr	bandwidth(VR("/VOUT1") 3 "low")	ymax(dB20(VR("/VOUT2")))	2.968M		<input checked="" type="checkbox"/>	<input type="checkbox"/>
bandwidth cascode	expr	bandwidth(VR("/VOUT2") 3 "low")		6.331M		<input checked="" type="checkbox"/>	<input type="checkbox"/>
gbw cs	expr	gainBwProd(VR("/VOUT1"))		22.84M		<input checked="" type="checkbox"/>	<input type="checkbox"/>
gbw cascode	expr	gainBwProd(VR("/VOUT2"))		53.27M		<input checked="" type="checkbox"/>	<input type="checkbox"/>
ugf cs	expr	unityGainFreq(VR("/VOUT1"))		24.41M		<input checked="" type="checkbox"/>	<input type="checkbox"/>
ugf cascode	expr	unityGainFreq(VR("/VOUT2"))		53.52M		<input checked="" type="checkbox"/>	<input type="checkbox"/>

Figure 18 results from adexl

	Common source	Cascode amplifier
Gain	7.678	8.391
Gain in dB	17.71	18.48
BW	2.968M	6.331M
GBW	22.84M	53.27M
UGF	24.41M	53.52M

Hand analysis:

$$|A_{VCS}| = g_{m1} * (r_o || RD) = g_{m1} * \left(\frac{1}{g_{ds}} || RD\right) = 202.3\mu * \left(\frac{1}{4.126\mu} || 45K\right) = 7.678$$

$$|A_{VCascode}| = g_{m1} * RD || (r_{o1} + r_{o2} + (g_{m2} + g_{mb2}) * r_{o1} * r_{o2})$$

$$= 191.1\mu * 45K || \left(\frac{1}{4.863\mu} + \frac{1}{4.842\mu} + (193.9\mu + 41.29\mu) * \frac{1}{4.863\mu} * \frac{1}{4.842\mu}\right) = 8.56$$

the dominant pole the input pole instead of the output pole. I will use miller theorem

$$BW_{CS} = \frac{1}{2\pi * R * (C_{GS} + C_{GD}(1+A))} = \frac{1}{2\pi * 10^6 * 10 * (1.633 * 10^{-15} + 418.4 * 10^{-18}(1+7.678))} = 3.024MHz$$

$$A_0 = -g_{m1} * (r_{o1} || R_{LFS})$$

$$R_{LFS} = \frac{1}{g_{m2}} \left(1 + \frac{RD}{r_{o2}}\right)$$

$$A_0 = 1.16$$

$$BW_{Cascode} = \frac{1}{2\pi * R * (C_{GS} + C_{GD}(1+A))} = \frac{1}{2\pi * 10^6 * 10 * (1.634 * 10^{-15} + 419.3 * 10^{-18}(1+1.16))} = 6.27MHz$$

$$GBW_{CS} = BW_{CS} * Gain_{CS} = 3.024M * 7.678 = 23.2MHz$$

$$GBW_{Cascode} = BW_{cascode} * Gain_{Cascode} = 6.27M * 8.56 = 53.67MHz$$

$$UGF \approx GBW$$

	Simulator	Hand analysis
Gain CS	7.678	7.678
Gain Cascode	8.391	8.56
BW CS	2.968M	3.024M
BW cascode	6.331M	6.27M
GBW CS	22.84M	23.2M
GBW Cascode	53.27M	53.67M
UGF CS	24.41M	23.2M
UGF Cascode	53.52M	53.67M

Comment:

I used to calculate bandwidth open circuit theorem and miller theorem

I noticed the cascode gain doesn't change higher than common source is almost equal because when R_D has small value it is parallel to output impedance, so gain almost did not change.

For bandwidth we have dominant pole is input pole and when adding cascode miller theorem effect decreases on the input pole thus causing extension in bandwidth, this is reason for different in bandwidth.