

## Part 1: Exploring Sizing Tradeoffs Using SA

- 1) We want to design a simple current mirror with the following specs.

Parameter	
Input Current	$10\mu A$
Output Current	$20\mu A$
% Change in Current for $\Delta V_{out}=1V$	$<10\%$
Current direction (source/sink)	Sink

**Answer the following:**

- 2) The % Change in current translates to a spec on the  $\lambda = 1/V_A$  of the device. How much is the required  $\lambda$ ?

$$I_D = \frac{K}{2} V_{OV}^2 (1 + \gamma V_{DS}) = \frac{K}{2} V_{OV}^2 (1 + \gamma V_{OUT})$$

$$\Delta I_D = \frac{K}{2} V_{OV}^2 \gamma \Delta V_{OUT}$$

$$\frac{\Delta I_D}{I_D} = \frac{\gamma \Delta V_{OUT}}{1 + \gamma V_{OUT}} \approx \gamma \Delta V_{OUT} \rightarrow \gamma = 0.1$$

- 3) Sinking current means which device type? NMOS or PMOS?  
NMOS.

- 4) The higher the  $g_m/I_D$  (the lower the  $V^*$ ) the higher the headroom (the available swing), but the larger the area. Examine this trade-off using SA as shown below. Report L and W vs Vstar.



The screenshot shows the SA (Sizing Assistant) interface for a current mirror design. The parameters and their values are as follows:

Parameter	Value
CMIRR_CLM	Save State
ID	10u
Vstar	100m : 200m
1/VA	0.1
VDS	0.9
VSB	0
Stack	1

Figure 1 setup of SA

 


Figure 2 plot w & l vs v\*

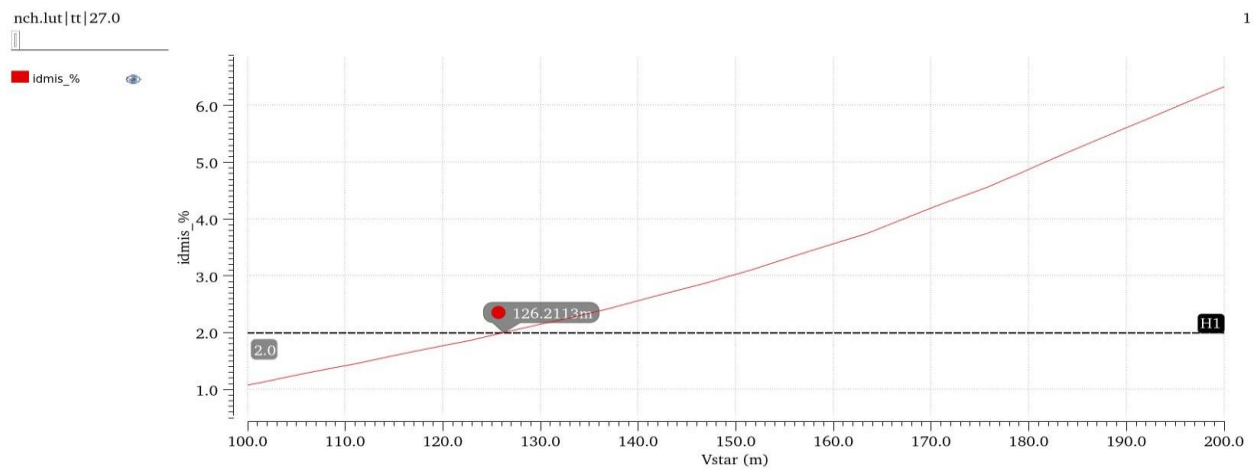


Figure 3 plot idmis vs vstar

- In my design I choose idmis = 2%, as shown in figure  $V^* = 126.2113mV$ .

 


Figure 4 get w & l at V\*

- ## Part 2: Current Mirror Simulation

- $V_{DS2} \approx V_{DS3} \approx V^* + 50mV \approx 126.2113m + 50m = 176.2113mV$ .
- $RB \approx \frac{V_{DS2}}{I_R} \approx \frac{176.2113m}{10u} \approx 17.6 K\Omega$  (range)

3

DC Analysis 'dc': R = (1 -> 30e+03)

1

 


Figure 6 get value of RB

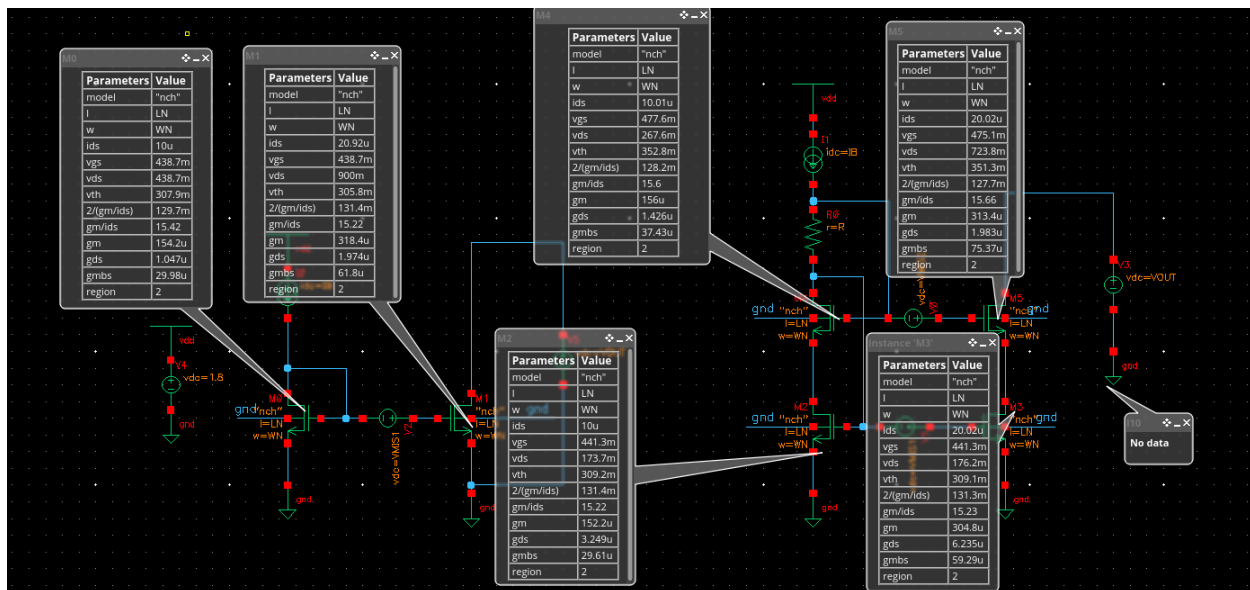


Figure 7 DC operating point

4) Do all transistors operate in saturation? Yes

## 2. DC Sweep ( $I_{out}$ vs $V_{OUT}$ )

 


Figure 8 plot  $i_{out}$  vs  $v_{out}$  of two current mirrors

- As shown from previous analysis that wide sense current mirror is more stable (constant current value) with voltage variations despite simple current mirror which changed with  $V_{OUT}$  variations, in the simple mirror the current increase when  $V_{OUT}$  ( $V_{DS}$ ) increases and exceed  $2 * I_B$  because  $V_{DS}$  isn't the same in M0 and M1 but in the second circuit they are the same that's why the current saturate.
- Because at this specific point,  $V_{DS}$  of the two mirror mosfets are the same so there won't be any mismatch error the mirroring will be more accurate as  $V_{DS}$  is the same and  $V_{GS}$  is the same.

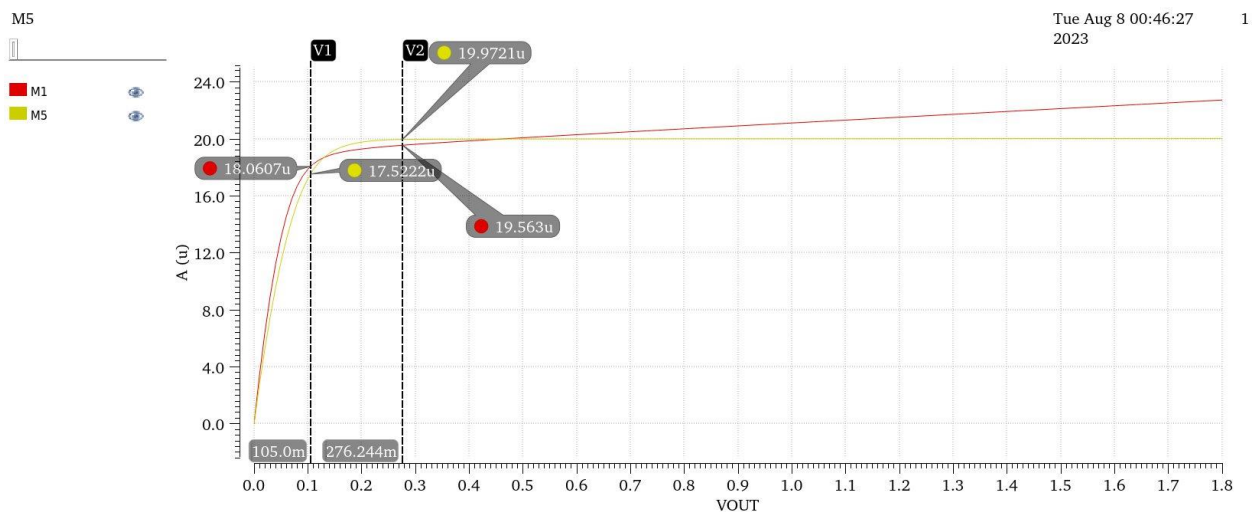


Figure 9 compliance from the plot

- as shown in figure compliance voltage of simple CM is approximately 105 mV and for wide swing CM is approximately 276.244 mV .

2)

 


Figure 10  $i_{out}$  at  $v_{out}$  equal 0.5 & 1.5

$$\text{percentage change} = \left( \frac{22.1361 - 20.0897}{20} \right) * 100 = 10\%$$

The Change in Current for  $\Delta V_{out} = 1V < 10\%$  from part 1.

3)

 


Figure 11 plot error of  $i_{out}$

- The wide-swing current mirror has better efficiency than the simple current mirror so the error in the wide-swing is less than the simple current mirror and the simple current mirror has lower  $R_{out}$ , and error of wide swing almost equal zero because the above 2 transistors make  $V_{DS}$  in the 2 transistors the same and have high output impedance.

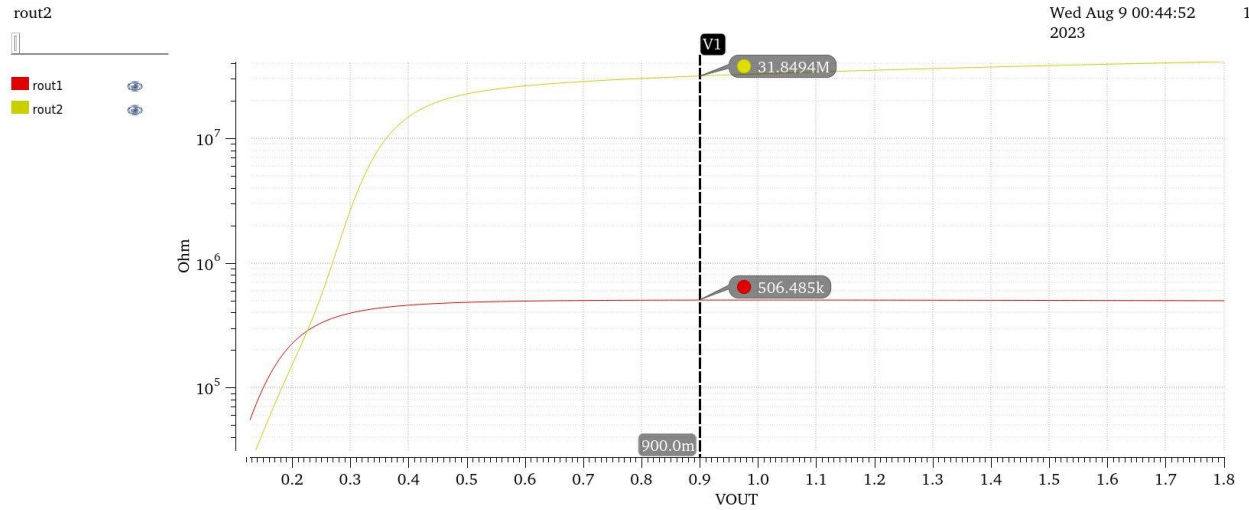


Figure 12 plot rout

- Rout of wide sense CM is more than that of simple CM because output of wide sense CM is cascaded which give high impedance while simple CM is only a single transistor, so its output impedance not boosted.
- yes, because  $V_{OUT}$  is the  $V_{DS}$  of the output mosfet so as  $V_{OUT}$  changes  $V_{DS}$  changes so the transistor either go deeper into saturation or towards the edge of saturation which will change the value of  $r_o$ .

Hand analysis:

$$R_{OUT_{Simple}} = r_{o1} = \frac{1}{g_{ds1}} = \frac{1}{1.974\mu} = 506.5K\Omega$$

$$R_{OUT_{Wide}} = r_{o5}(1 + (gm_5 + gmb_5)r_{o3}) = 31.9M\Omega$$

	Simulator	Analytical
Simple CM	506.485K $\Omega$	506.5K $\Omega$
Wide swing CM	31.849M $\Omega$	31.9M $\Omega$

### 3. Mismatch

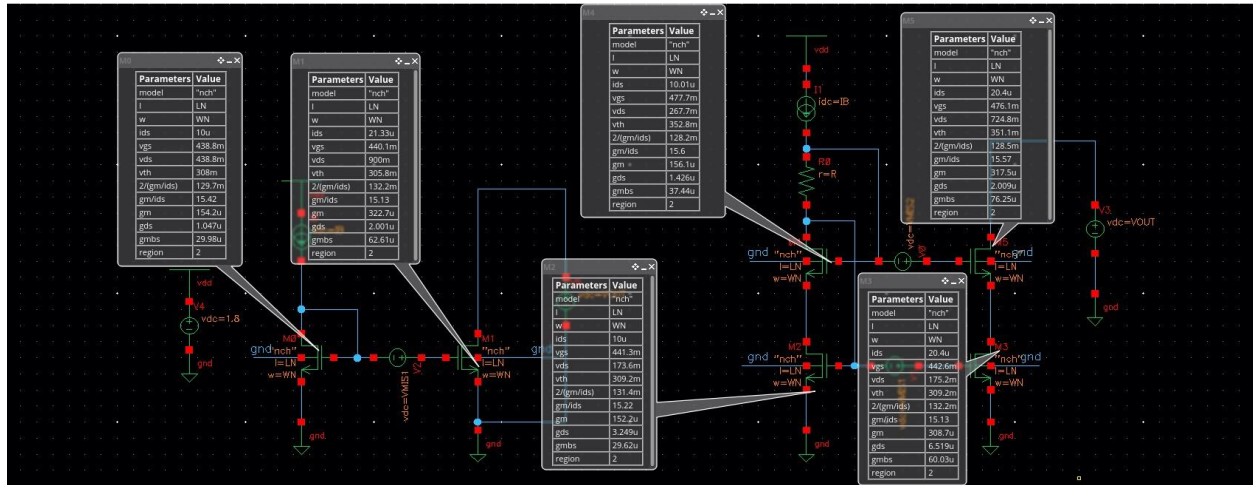


Figure 13 DC operating point at vmis1

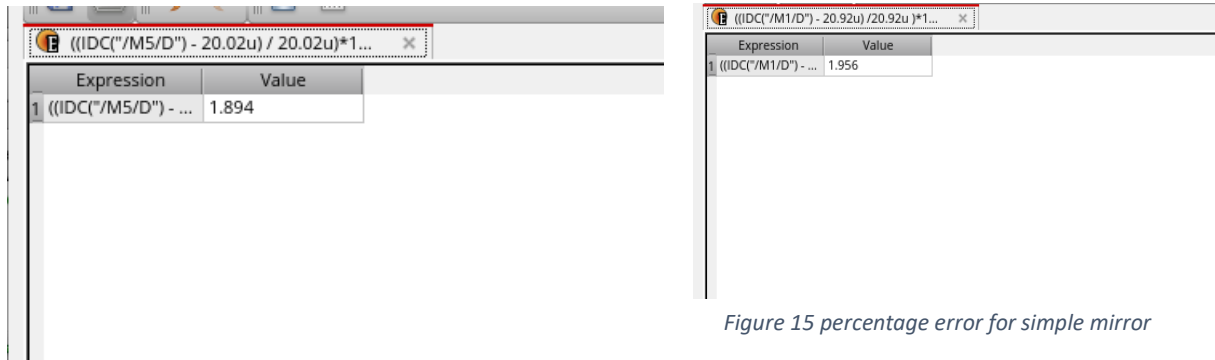


Figure 15 percentage error for simple mirror

Figure 14 percentage error from simulation for wide swing

$$\Delta I = G_M \Delta V = g_m \Delta V = \frac{2 I_D \Delta V}{V^*}$$

$$\frac{\Delta I}{I} = \frac{2 \Delta V}{V^*} = \frac{2 \cdot V_{MIS}}{V^*} * 100 = 2\%$$

	Simulator	Analytical
Percentage error wide swing	1.894%	2%
Percentage error simple	1.956%	2%



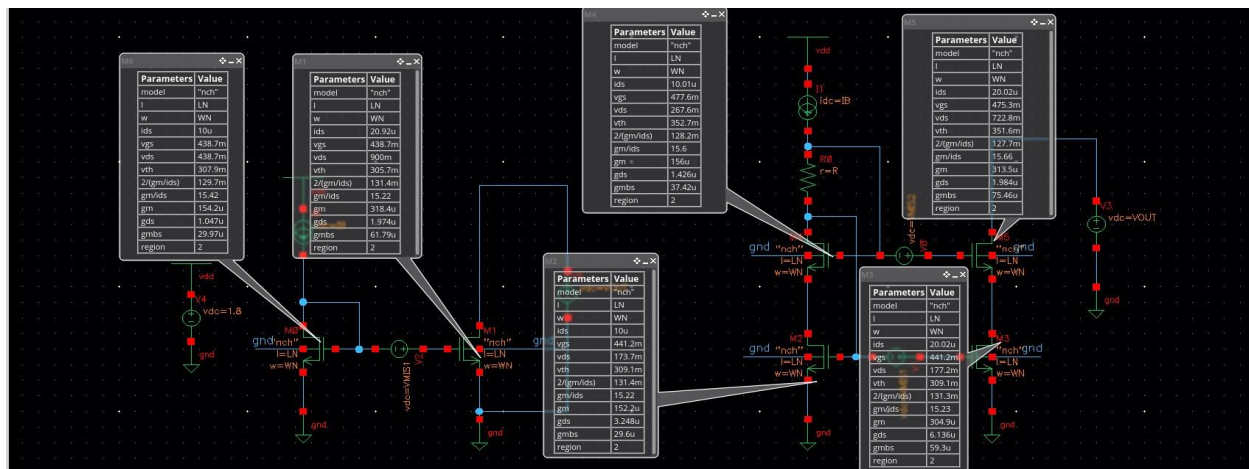


Figure 15 DC operating point at vmis2

 


Figure 16 result of error

$$\frac{\Delta I}{I} = G_M \Delta V = \frac{gm_5}{(1 + (gm_5 + gmb_5)r_{o3})} * \frac{V_{MIS2}}{I} * 100 = 0.03\%$$

	Simulator	Analytical
Percentage error	0.01%	0.03%

5-In simple mirror because the mismatch affects  $V_{GS}$  (strong volt), and  $I$  change directly but in the second cascode wide swing mirror the mismatch affects  $V_{DS}$  (the weakest volt).

6-For the mirror we should make it larger to increase the area and the mismatch decrease.