

## Part 1: sizing chart

- First get value of  $R_D = \frac{V_{RD}}{I_D}$   $V_{RD} = V_{DD}/2 = 0.9V$   $I_D = 100\mu A$

Then  $R_D = 6k\Omega$

- we can get gain is given by:

$$|A_v| \approx gmR_D = \frac{2 * I_D * R_D}{V_{OV}} = \frac{2 * V_{RD}}{V_{OV}}$$

But for real mosfet  $V_{OV} \neq \frac{2 * I_D}{gm}$  we define new expression  $V^* = \frac{2 * I_D}{gm}$

- For a square-law device,  $V^* = V_{OV}$ , however for a real MOSFET they are not equal. The actual gain is now given by  $|A_v| \approx \frac{2 * V_{RD}}{V^*}$

- we have  $|A_v| = 6$  then  $V^* = \frac{2 * V_{RD}}{A_v} = \frac{2 * 0.9}{8} = 225mV$ , which we make the operating point voltage of real MOSFET overdrive voltage  $V_Q^* = 225mV$ .

- And we assume that channel length value will be  $L = 2\mu m$ , to avoid short channel effects.

- By using sizing assistant, we have this parameter:

$$L = 2\mu m$$

$$I_D = 100\mu A$$

$$V^* = 225mV \quad gm = \frac{2 * I_D}{V^*} = \frac{2 * 100\mu}{225m} = 888.88\mu S$$

$$V_{DS} = 0.9V \quad V_{SB} = 0V$$

After using sizing assistant, the value of other parameters generated

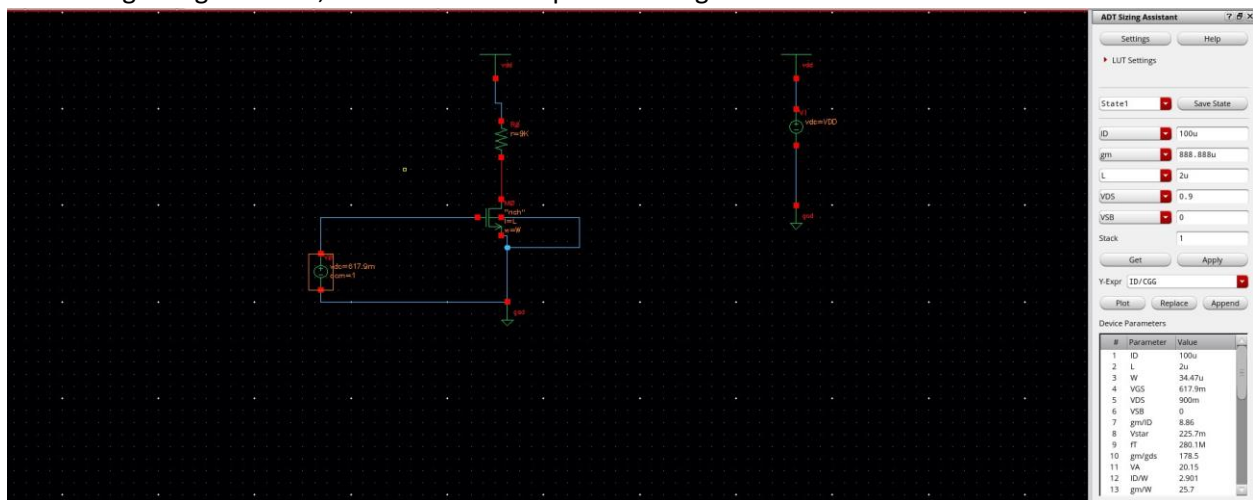


Figure 1 results of sizing assistant

By applying AC analysis, we get this result and use parameters of sizing assistant.

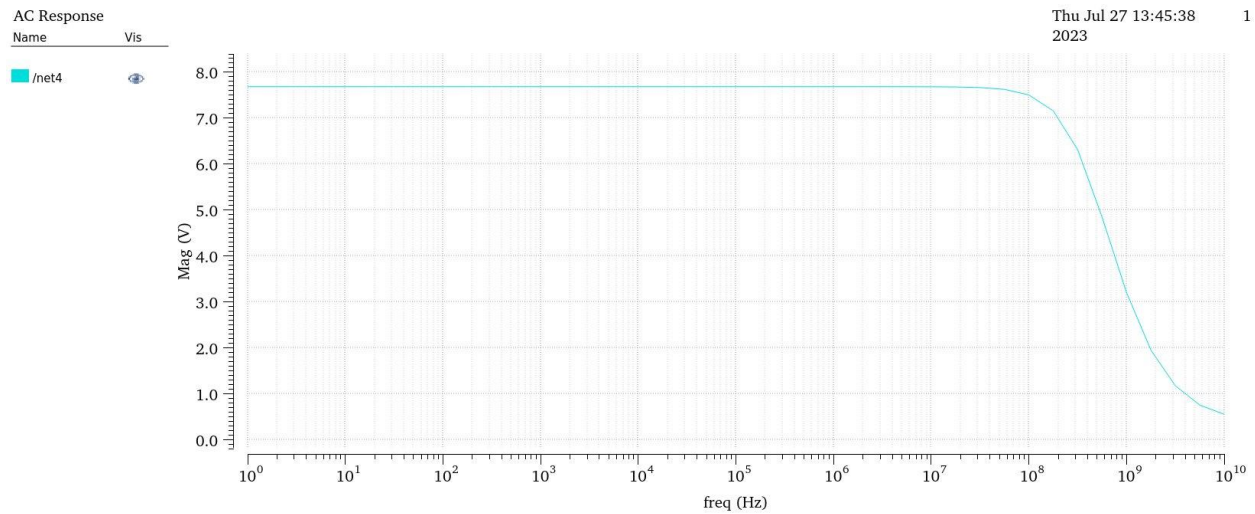


Figure 2 AC analysis to get value of the gain

As shown on figure DC gain = 7.6 , I want the gain to be 8 by increasing the value of gm gain will be increased

$$A_v = -gm * (r_o || RD)$$

By increasing gm to  $950\mu S$  and decreasing  $V^*$  to 211.6mV

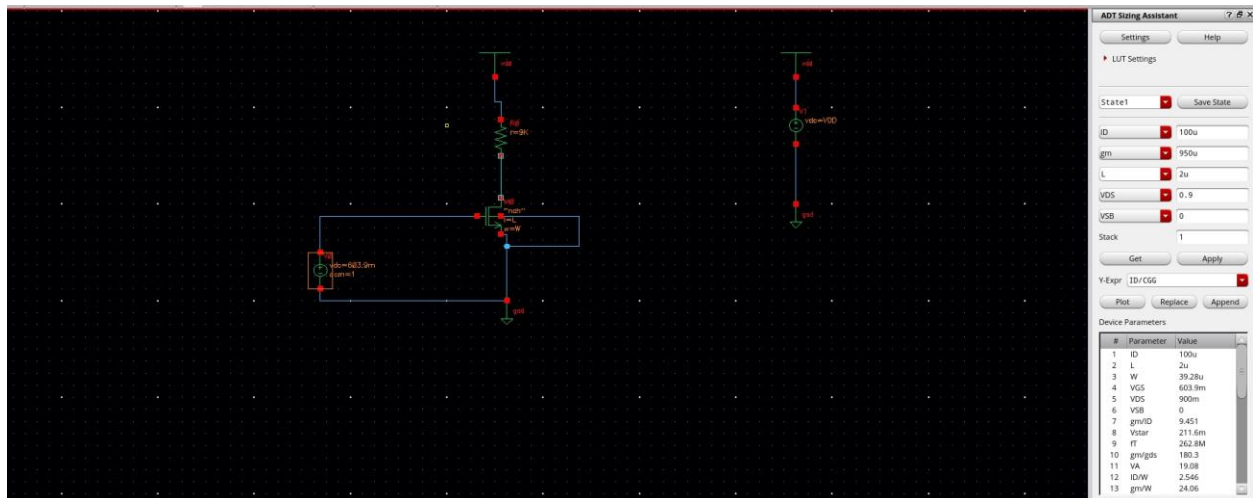


Figure 3 sizing assistant results gm=950u results

When I used the parameters  $W=39.28\mu m$  and  $V_{GS} = 603.9mV$  DC gain will equal 8 as shown below.

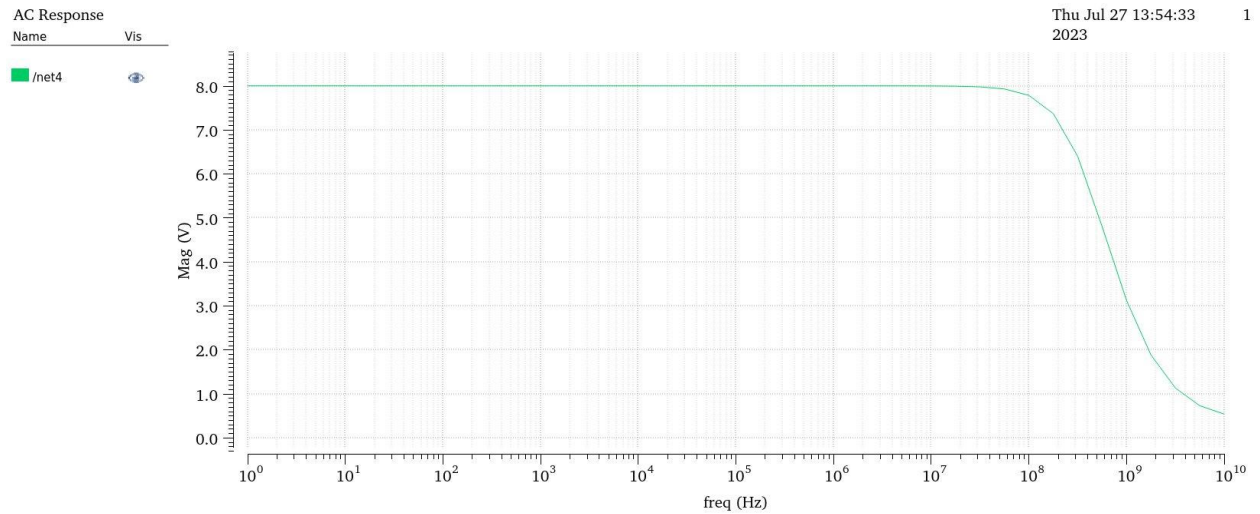


Figure 4 AC analysis to get gain.

Get DC operating point.

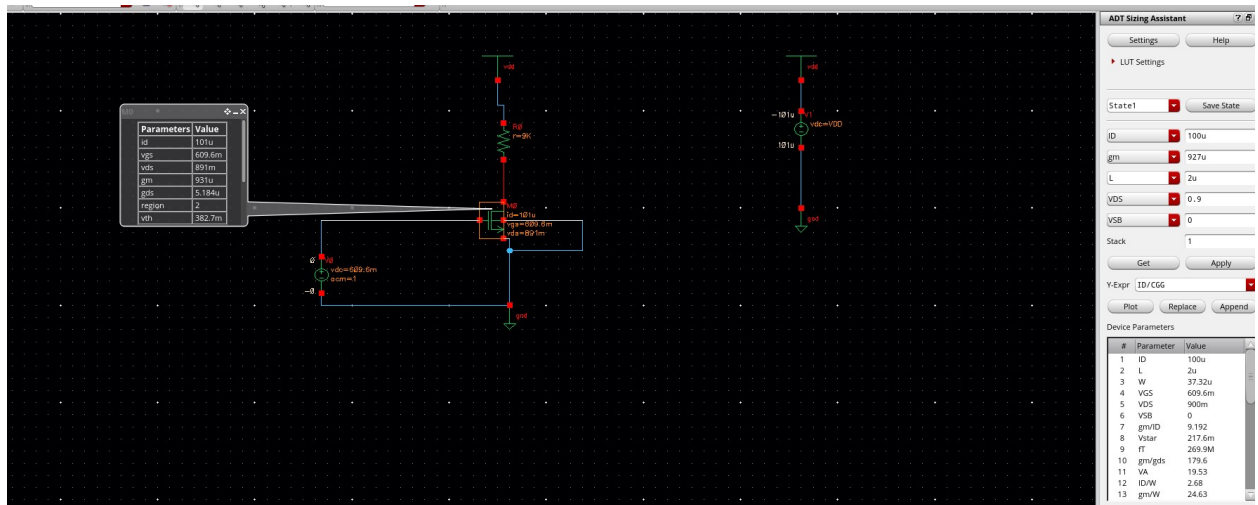


Figure 5 DC operating point

gm	931μS
gds	5.84μS
Vth	382.7mV

$$A_v = -g_m * (r_o || R_D) = -931\mu * (9K || \frac{1}{5.184\mu}) = -8.005$$

## Part 2: CS Amplifier

### 1. OP and AC Analysis

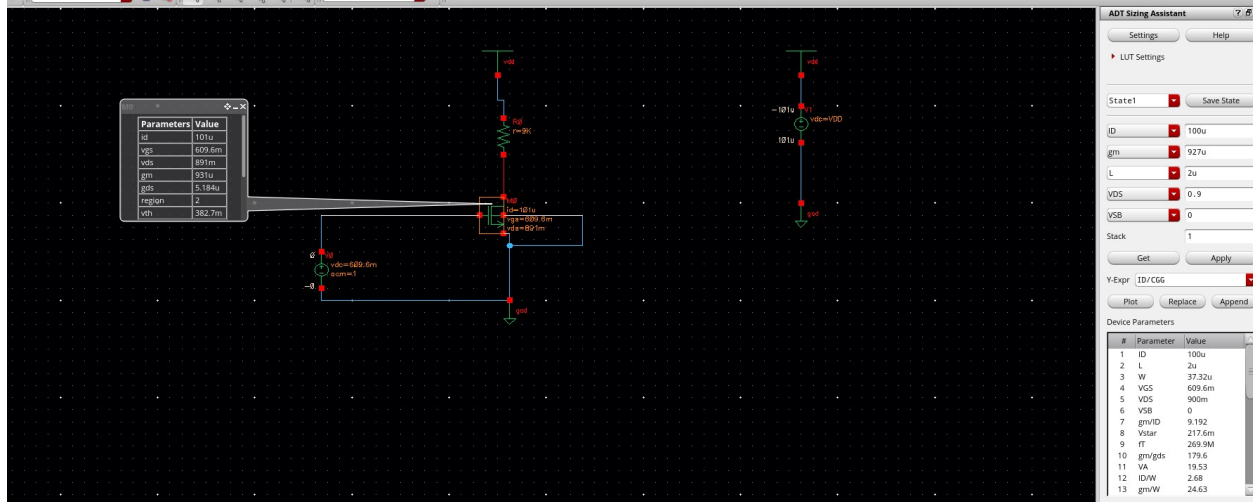


Figure 6 operating point in cs amplifier

Parameter	CS amplifier
$I_D$	$101\mu A$
$g_m$	$931\mu S$
$g_{ds}$	$5.184\mu S$
$r_o$	$192.901K\Omega$
$V_{GSQ}$	$609.6mV$

- From these results we found that there is a great agreement between our results in part 1 and CS amplifier simulation part and region of MOSFET equal 2 which mean that MOSFET is in saturation region.

3)  $r_o = 192.901K\Omega \gg RD = 9K\Omega$

$R_{OUT} = r_o || RD \cong 8.6K\Omega$  which is very close to  $RD$  we can neglect value of  $r_o$ .

- if we minimum channel length the value of  $r_o$  will decrease following the relation  $r_o = \frac{1}{\lambda I_{DS}}$

and  $\lambda \propto \frac{1}{L} \therefore r_o \propto L$ . the error will not remain the same, and  $r_o$  will be smaller and the error will be larger.

- Intrinsic gain of MOSFET will be:

$$A_v = -g_m * r_o = -950\mu * 192.901K = -183.255$$

- Amplifier gain analytically:

$$A_v = -g_m * (r_o || RD) = -8.005.$$

From these calculations we found that intrinsic gain is greater than amplifier gain



$\therefore$  intrinsic gain  $\gg$  amplifier gain.

•From simulation we can find DC gain:

DC gain =8.005

DC gain in dB =18.07

This values meets specs .

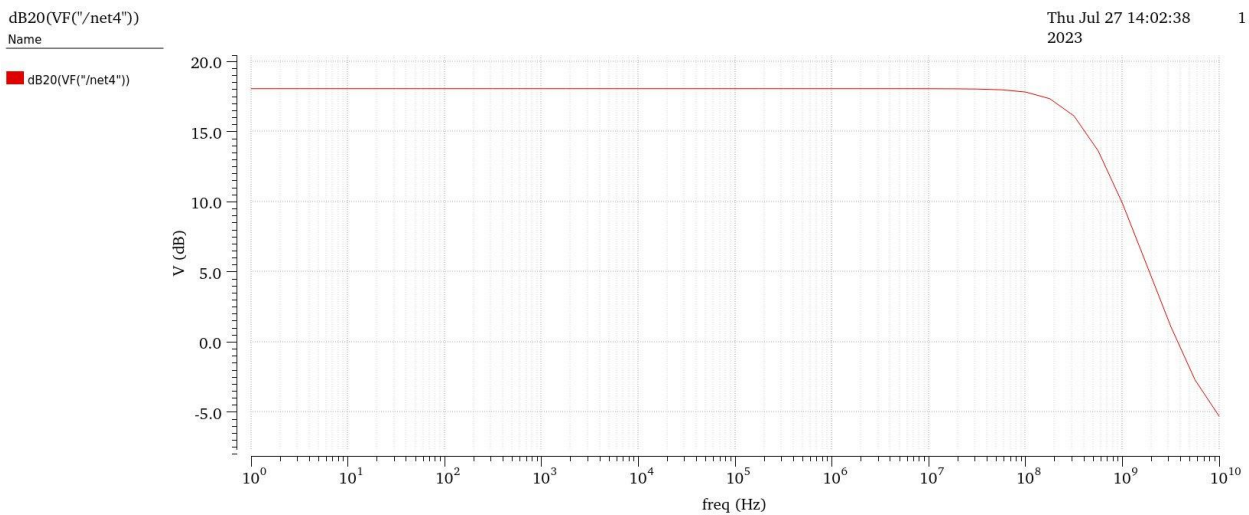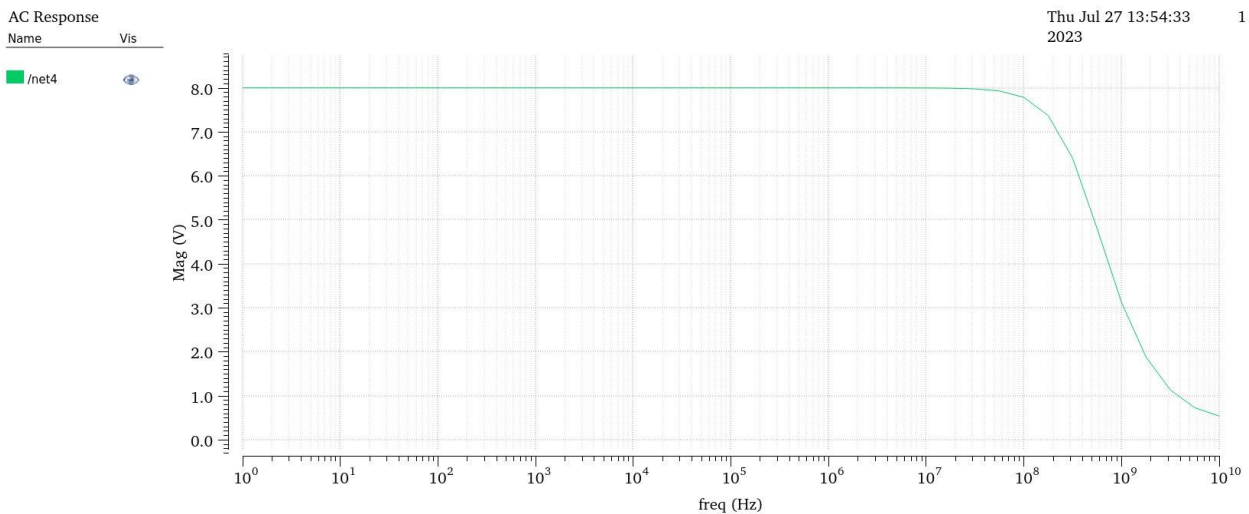

Name	Type	Details	Value	Plot	Save	Spec
gain	signal	/vout		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
gain in dB	expr	dB20(VF("/vout"))		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
DC gain	expr	ymax(mag(VF("/vout")))	8.005	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
DC gain in dB	expr	ymax(dB20(VF("/vout")))	18.07	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Figure 9 values of gain from simulator

## 2. Gain Non-Linearity

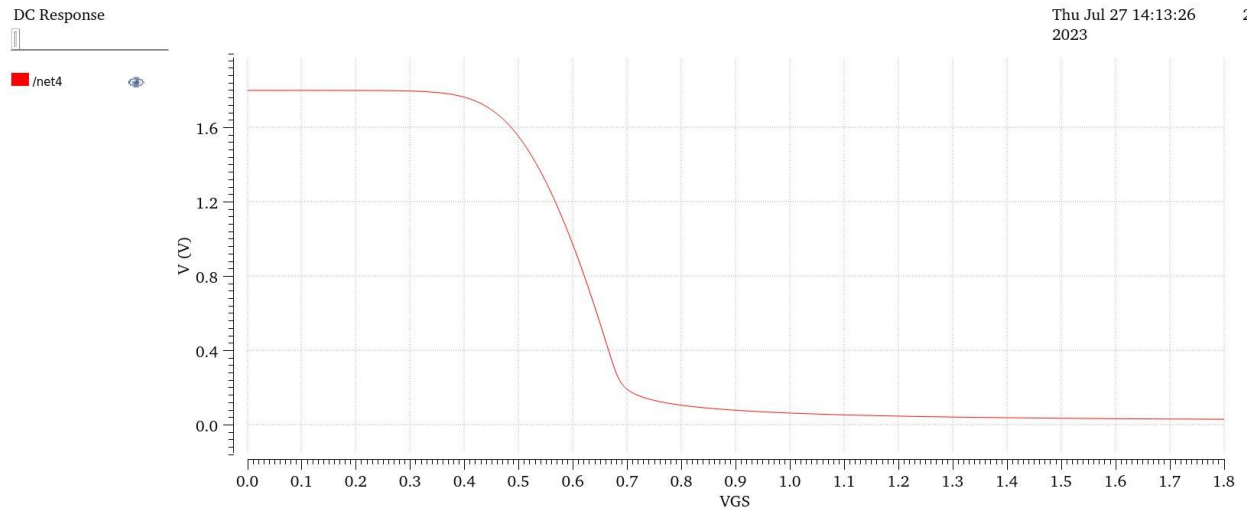


Figure 10  $V_{out}$  Vs  $V_{in}$  in DC Sweep

- this is a nonlinear relation as  $V_{OUT} = V_{DD} - I_R$  is which depends on current whose relation depends on region of operation hence  $V_{in}$  and you know  $I$  depend on  $V_{in} = V_{gs}$

$$I_D = \left(\frac{1}{2}\right) \left(\frac{W}{L}\right) \mu C_{ox} (V_{gs} - V_{th})^2.$$

with quadratic relation in saturation that's why it is nonlinear.

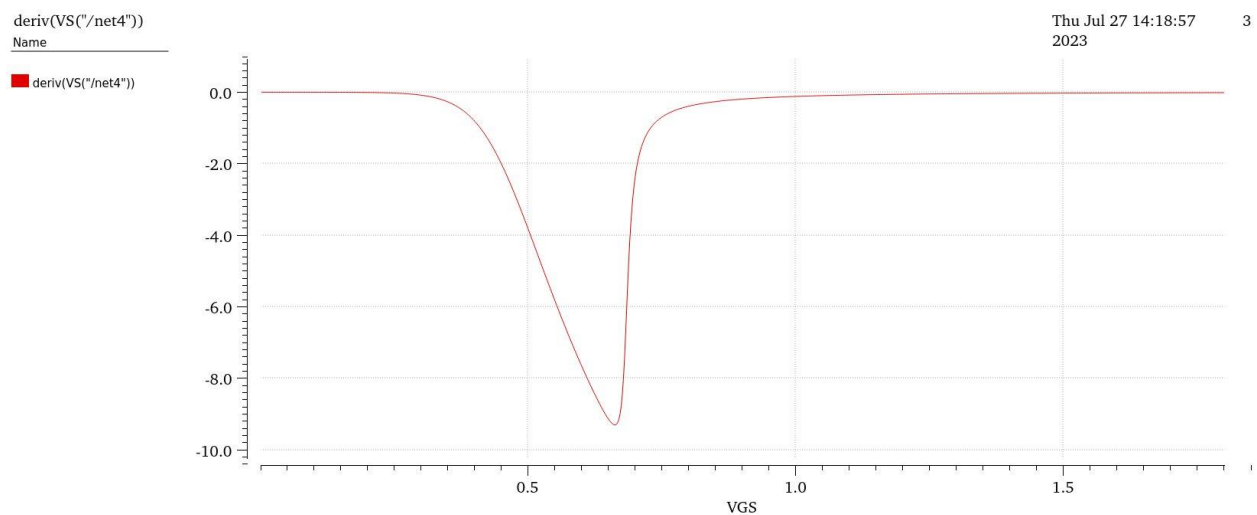


Figure 11 derivative of  $V_{out}$  vs  $V_{in}$

- The figure shown in Figure indicates that the derivative of  $V_{OUT}$  is not a constant value. This is because the relationship between  $V_{OUT}$  and  $V_{in}$  is not linear, as it depends on the current that depend on which region of operation, is dependent on  $V_{GS}$ .

## Transient analysis:

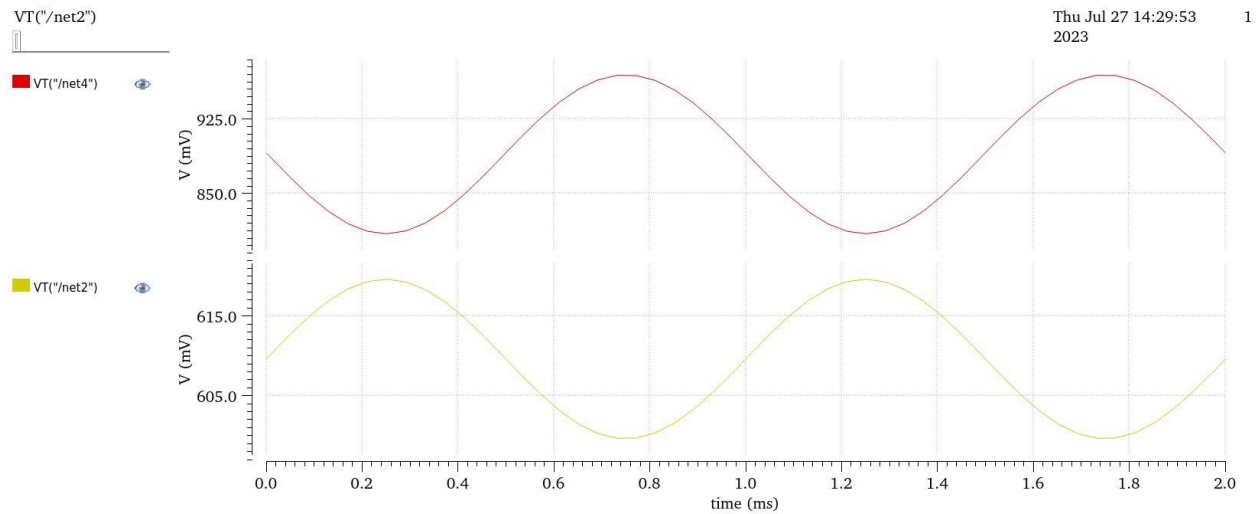


Figure 12 transient analysis of  $V_{out}$  and  $V_{in}$

## Plot gm in transient analysis

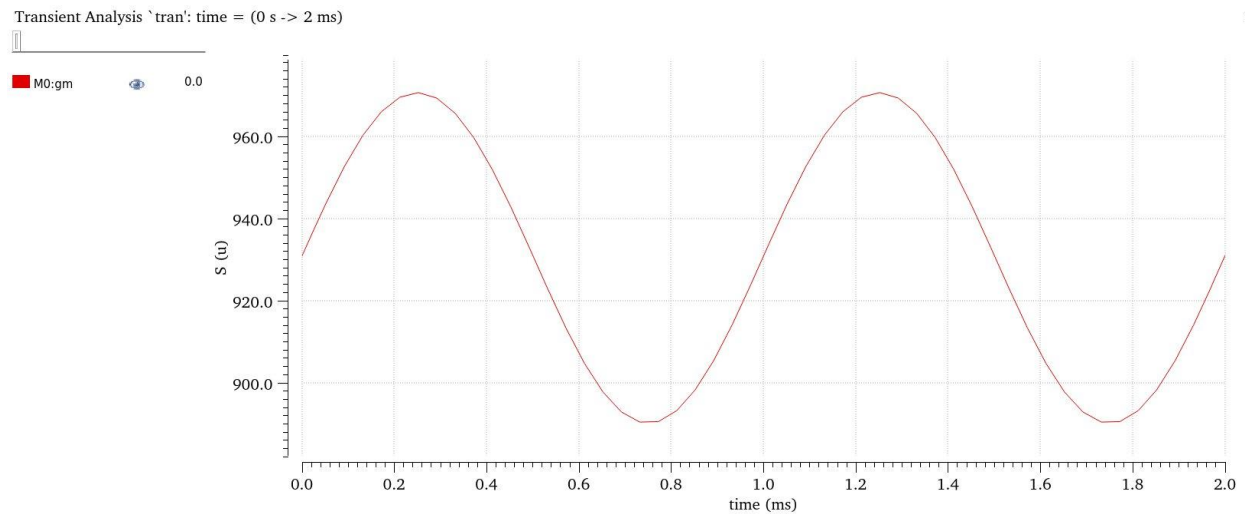


Figure 13 plot  $g_m$  in transient analysis

5) as shown figure, the variation of  $g_m$  over time demonstrates that  $g_m$  is dependent on the input voltage  $V_{GS}$ , which in turn is time dependent. Therefore,  $g_m$  exhibits a strong dependence on the input voltage  $V_{GS}$ .

6) Based on the previous analysis, it is evident that our amplifier is a non-linear amplifier due to the non-linear relationship between its input voltage and output voltage. This non-linearity arises from the dependence of the amplifier's gain on  $g_m$ , which is heavily strongly by the input voltage  $V_{GS}$ . As a result, the non-linear dependence of  $g_m$  on  $V_{GS}$  leads to non-linearity in the amplifier's gain.



### 3. [Optional] Maximum Gain

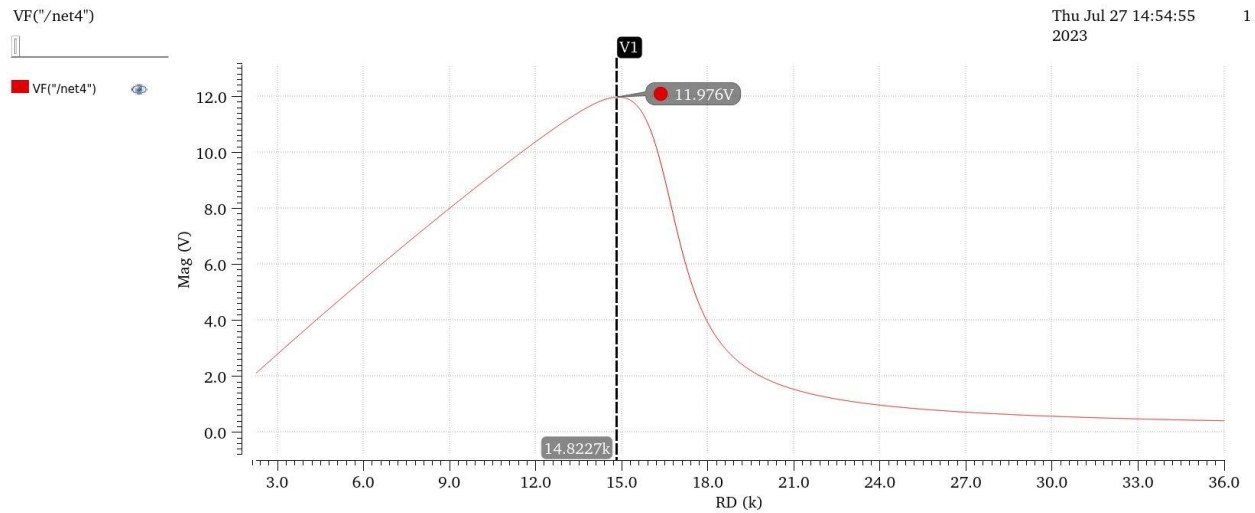


Figure 14 AC analysis plot  $V_{out}$  vs  $R_D$

As shown in the figure the gain increased with  $R_D$  then decreased at certain point, because I have constant current as  $R_D$  increases at certain point, I will be entering the triode region then gain will decrease.

From the simulator highest  $R_D = 14.8227\text{K}\Omega$  this gives you max gain = 11.976

Hand analysis:

$$A_v = -g_m * (r_o || R_D) = -g_m * \frac{r_o * R_D}{r_o + R_D}$$

I have  $I_D = 100\mu\text{A}$  and  $v^* = 225\text{mV}$  then  $V_{RD} = 1.8 - 0.225 = 1.575\text{V}$

$$R_{D_{max}} = 15.75\text{K}\Omega$$

$$A_v = -g_m * (r_o || R_D) = -931\mu * \frac{192.901\text{K} * 15.75\text{K}}{192.901\text{K} + 15.75\text{K}} = 13.55$$

	Simulator	Hand analysis
$R_D$	14.8227K $\Omega$	15.75K $\Omega$
Gain	11.976	13.55

Output signal swing:

$$V_{out_{max}} = V_{DD} = 1.8\text{V}$$

$$V_{out_{min}} = V_{OV} \cong V^* = 225\text{mV}$$



I have tried out to get max swing I put sinusoidal input signal =125mv results below

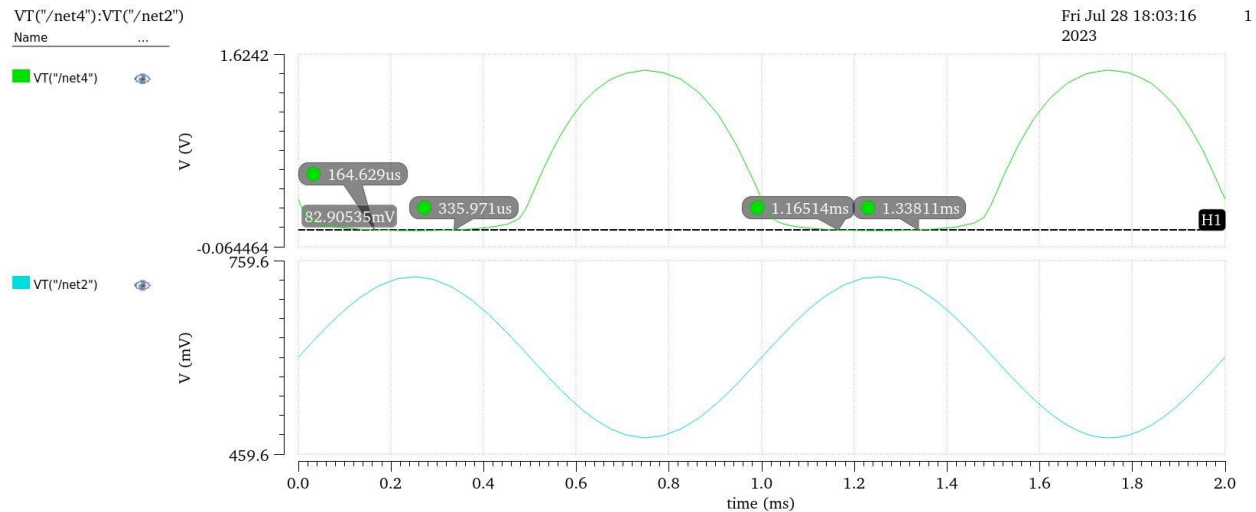


Figure 15 transient analysis at input 125Mv

As shown on above figure I have exceed minimum range (225 mV) the  $V_{out\_min\_graph} = 82.9mV$

To make it in the range, decrease the input signal, I have tried out with different values of input until get max sinusoidal signal =11.5mV.

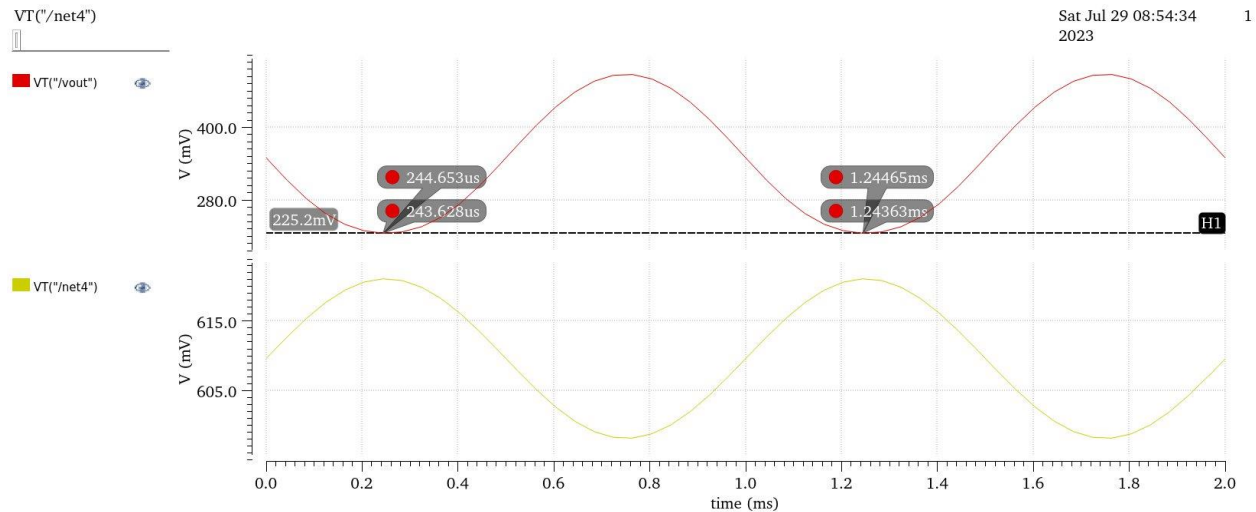


Figure 16 Ttransient analysis at 11.5mV input

. I have get vout to minimum value 225.2mV at input 11.5mV

8)No, Certainly, when scaling down the supply voltage in a power amplifier while keeping the drain current ( $I_D$ ) constant, the value of  $R_D$  that leads to the edge of saturation will decrease. Consequently, the maximum achievable gain of the amplifier will also decrease. Additionally, the reduced supply voltage will limit the maximum available output voltage swing. As a result, this limitation can have a negative impact on the overall gain of the amplifier.

#### 4. [Optional] Gain Linearization (feedback)

By using sizing assistant with parameters for PMOS Like NMOS of part one

$$L=2\mu m \quad I_D=100\mu A$$

$$g_m = 950\mu S \quad V_{DS} = 0.9V \quad V_{SB} = 0V$$

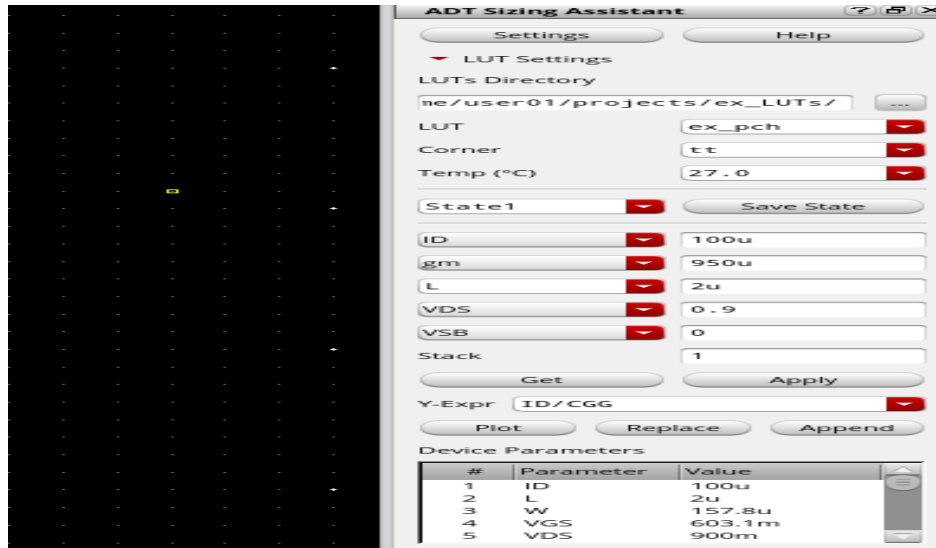


Figure 17 PMOS SIZING

As shown in figure sizing assistant generate  $W=157.8\mu m$  and  $V_{GS} = 603.1mV$ .

$$A_v = \frac{R_F}{R_{in}} = 8 \text{ then } R_F = 1M\Omega.$$

7) the two curves cross at 619.355mV which is nearly to  $V_{GS}$  for NMOS =619.9mV, because of no current flows through resistor at point  $V_{Ouy} = V_{IN}$ .

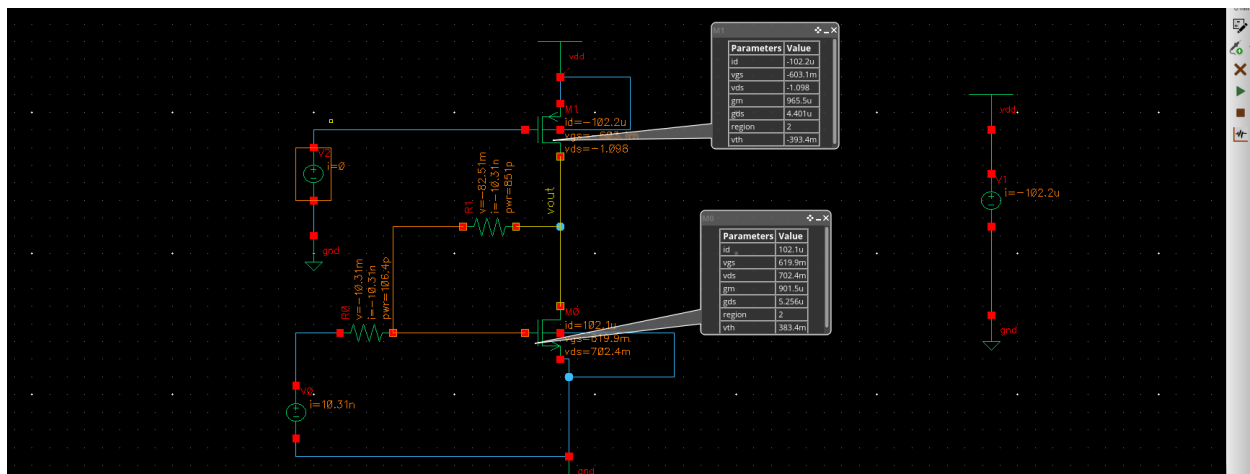


Figure 18 DC operating point

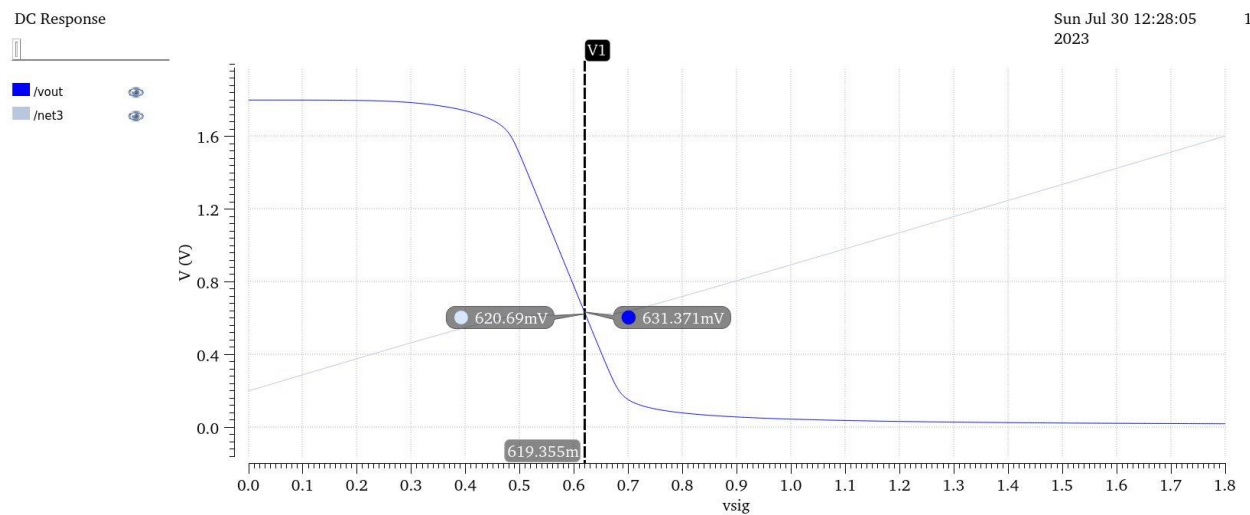


Figure 19 plot vout and vin vs Vsigt

8)yes, in saturation region  $V_{OUT}$  is linear to  $V_{sig}$  due to presence the feedback resistor

Calculate new gain:

$$R_{OUT} = r_{o1} || r_{o2} || (R_F + R_S) || \frac{R_F + R_S}{g_{m1} R_S}$$

$$GM = \frac{1 - g_{m1} R_F}{R_F + R_S}$$

$$\text{Gain} = GM * R_{OUT}$$

From relations gain is linear in sat region.

Why gain is linear? Because gm is this region nearly constant thus the gain linear shown in figures below.

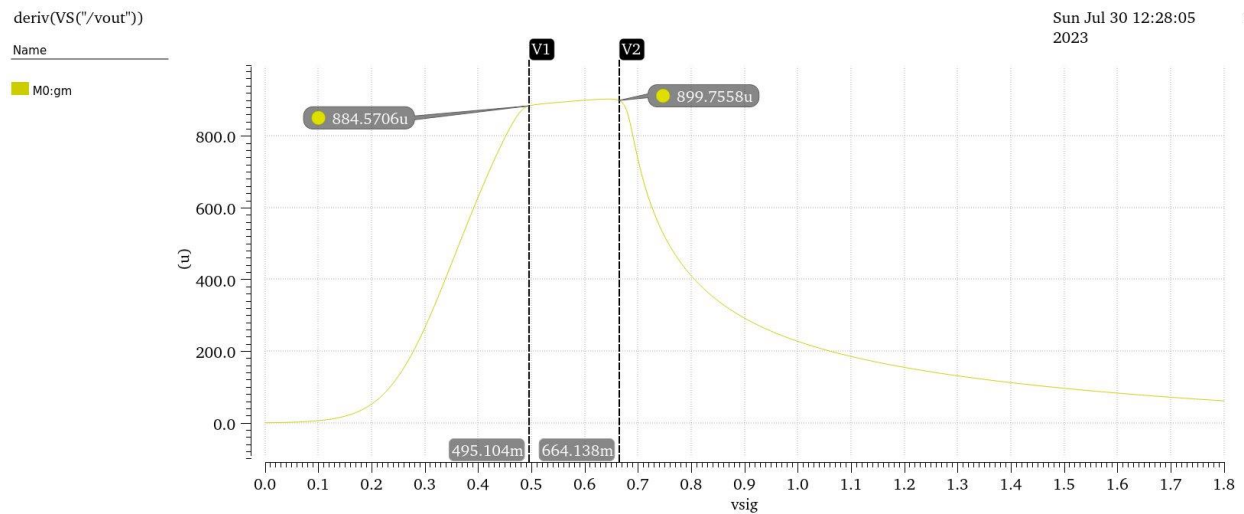


Figure 21 plot gm vs Vsig at sat region

- these two graphs show gm is nearly constant at sat region and gain is linear in sat region.

9) the derivative of vout is constant at saturation region because in this region gain is linear because

Using feedback resistor, gm is constant in sat region, no variations with input swing.

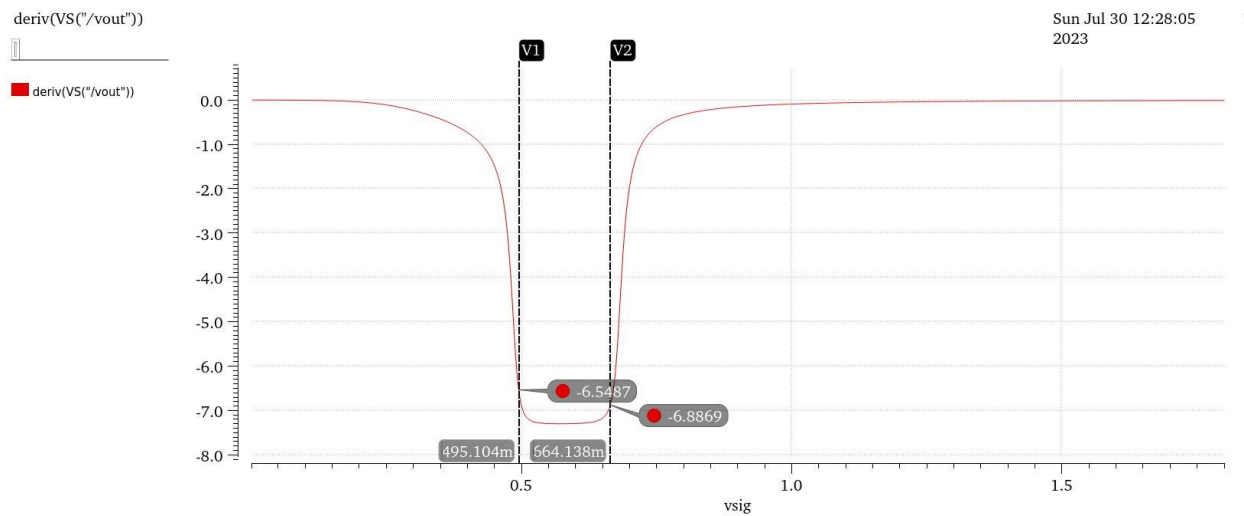


Figure 22 plot derivative of gm vs Vsig and regions

10) from 495.104mV to 664.138mV.

Range=664.138m -495.104m =0.17V

11)  $V^* < V_{OUT} < V_{DD} - V^*$  From part one I have used  $V^* = 211.6mV$

$211.6m < V_{OUT} < 1.8 - 211.6m.$

DC input Range  $= \frac{V_{DD} - 2*V^*}{A_v} = \frac{1.8 - 2*0.211}{8} = 0.172$

	Simulator	Analytical
Range	0.17 V	0.17 V