

## Part 1: sizing chart

- we can get gain is given by:

$$|A_v| \approx gmr_o = \frac{2 * I_D * V_A}{V_{OV} * I_D} = \frac{2 * V_A}{V_{OV}}$$

But for real mosfet  $V_{OV} \neq \frac{2 * I_D}{gm}$  we define new expression  $V^* = \frac{2 * I_D}{gm}$

- For a square-law device,  $V^* = V_{OV}$ , however for a real MOSFET they are not equal. The actual gain is now given by  $|A_v| \approx \frac{2 * V_A}{V^*}$

- we have  $V^* = 160mV$ .

- And we assume that channel length value will be  $L=0.5\mu m$  and  $W=10\mu m$ , to avoid short channel effects.

- from LAB01 we can get value of  $V_{TH}$  for NMOS

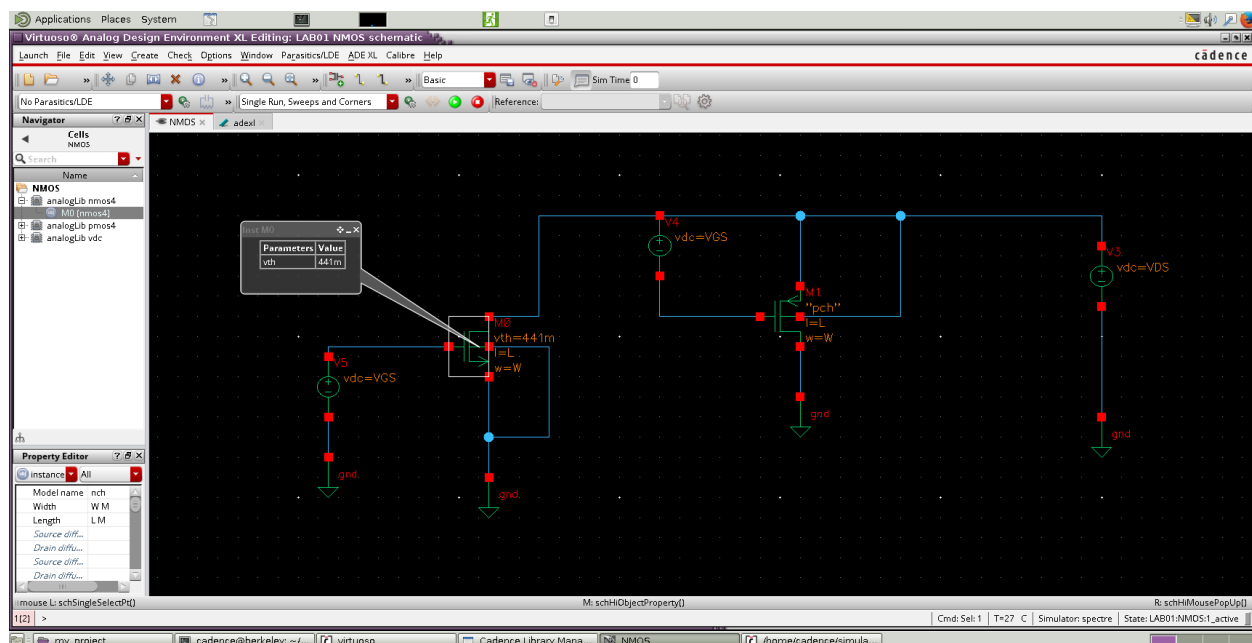


Figure 1 get value of  $V_{th}$  from simulation

- from simulation  $V_{TH} = 441mV$
- Sweep  $V_{GS}$  from 0 to  $\approx V_{TH} + 0.4V$   $0 \rightarrow 841mV$  with 10mV step. Set  $V_{DS} = \frac{V_{DD}}{2} = 0.9V$ .
- Sweep  $V^*$  and  $V_{OV}$  versus  $V_{GS}$  on same plot .

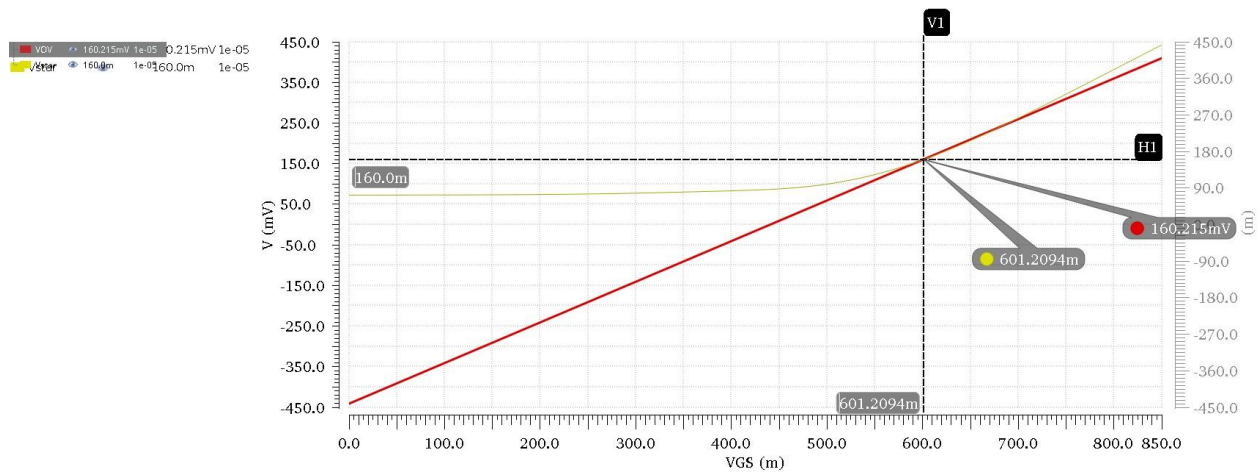


Figure 2 simulation  $V^*$  and  $V_{ov}$  vs  $V_{GS}$

- from simulation we found at  $V_{GSQ} = 601.2094mV$ ,  $V_{OVQ} = 160.215mV$ ,  $V_Q^* = 160mV$ .
- plot  $I_D$  &  $g_m$  and  $g_{ds}$  versus  $V_{GS}$ :

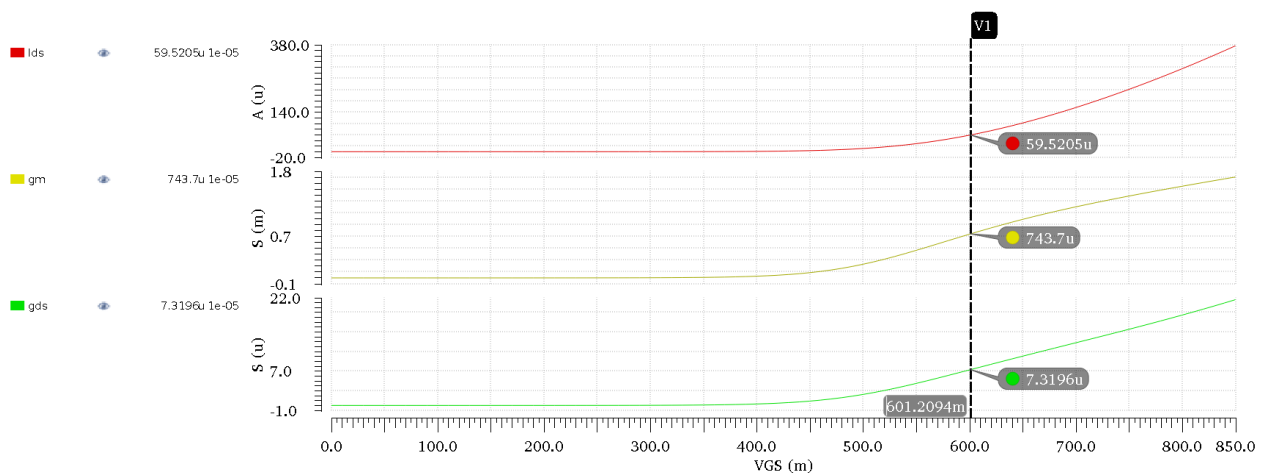


Figure 3 plot  $I_D$  &  $g_m$  and  $g_{ds}$  versus  $V_{GS}$ :

| Parameter | Simulator value |
|-----------|-----------------|
| $V_{OVQ}$ | 160.215mV       |
| $V_Q^*$   | 160mV           |
| $I_{DQ}$  | 59.5205 $\mu A$ |
| $g_{mQ}$  | 743.7 $\mu S$   |
| $g_{dsQ}$ | 7.3196 $\mu S$  |

- I want current equal 150 $\mu A$  but at  $W=10\mu m$   $I_{DQ} = 49.66\mu A$

| $W$        | $I_D$           |
|------------|-----------------|
| 10 $\mu m$ | 59.5205 $\mu A$ |
| ?          | 15 $\mu A$      |

Then  $W = \frac{15\mu \cdot 10\mu}{59.5205\mu} = 2.52\mu m$ .

- get parameters at this W:

$$\frac{gm}{gm_Q} = \frac{W}{W_Q} \quad \frac{gm}{743.7\mu} = \frac{2.52}{10} \quad gm = 187.4124\mu S$$

$$\frac{g_{ds}}{g_{ds_Q}} = \frac{W}{W_Q} \quad \frac{g_{ds}}{7.3196\mu} = \frac{2.52}{10} \quad g_{ds} = 1.845\mu S$$

$$I_D = 15\mu A$$

$$r_o = \frac{1}{g_{ds}} = 542.141K\Omega$$

So common source parameters are:

| Parameter | Value             |
|-----------|-------------------|
| L         | 0.5 $\mu m$       |
| W         | 2.52 $\mu m$      |
| $V_{GSQ}$ | 601.2094mV        |
| $I_D$     | 15 $\mu A$        |
| gm        | 187.4124 $\mu S$  |
| gds       | 1.845 $\mu S$     |
| $r_o$     | 542.141K $\Omega$ |

## Part 2: Cascode for Gain:

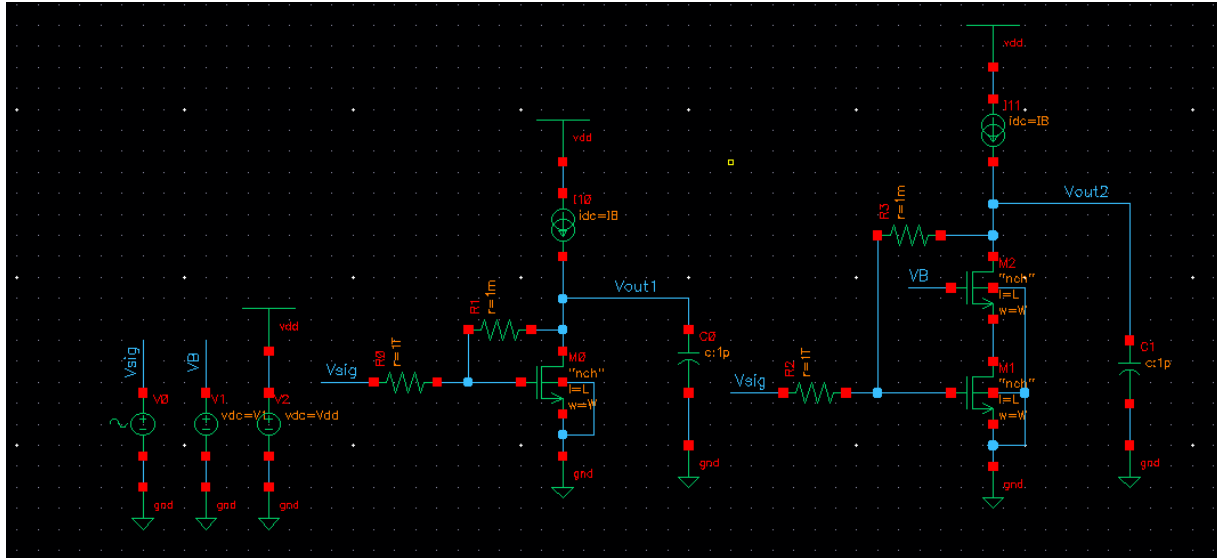


Figure 4 Cascode circuit schematic

- Select value of voltage bias for M1 mosfet :

$$V_{DS} \approx V^* + 100mV = 160m + 100m = 260mV.$$

By making sweep of  $V_{DS}$  versus  $V_B$  to get value of voltage bias .

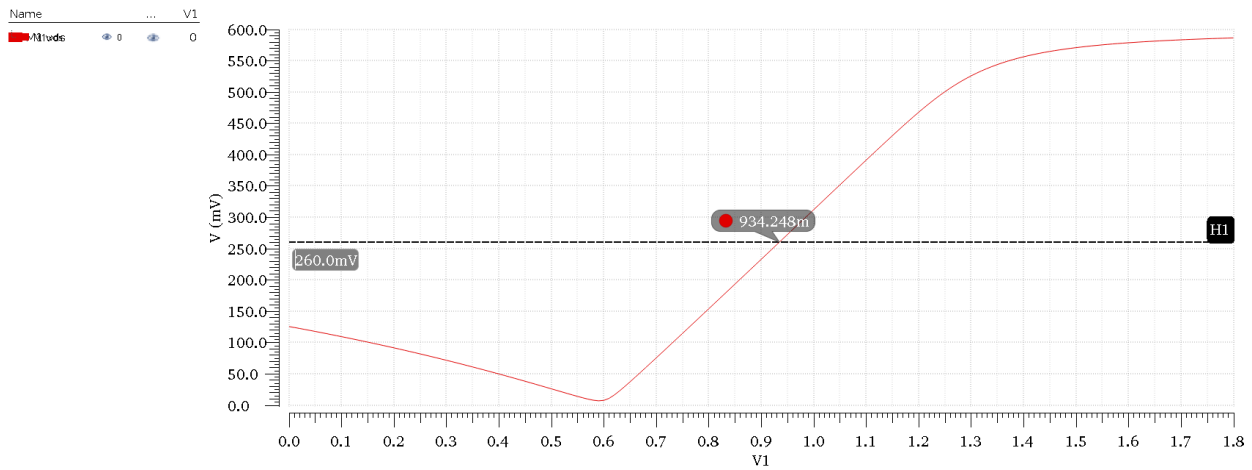


Figure 5 plot vds for M1 versus VB

•  $V_B = 934.248mV$ .

• DC operating point for CS and cascode amplifiers:

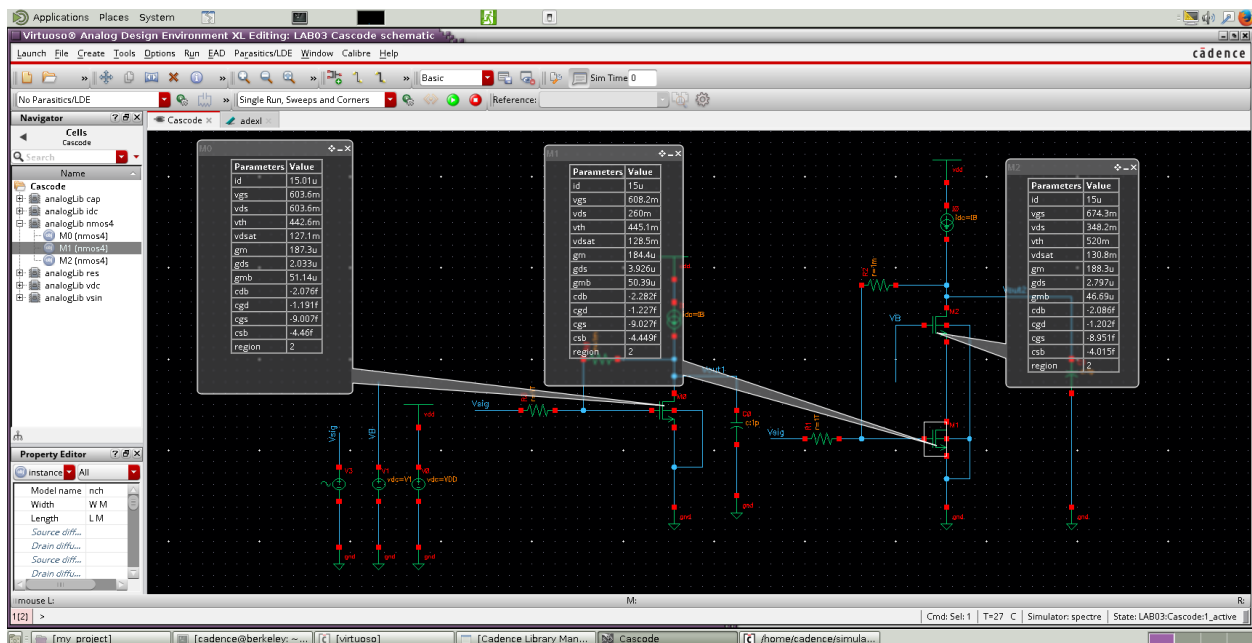


Figure 6 operating point parameters from simulation

5) as shown in fig (6) all transistors in region 2 (saturation region).

6) All transistors don't have the same threshold voltage even they have the same channel length L, this due to body effect as shown in fig (6) we notice that M0 and M1 have  $V_{TH}$  is almost the same, but M2 have different  $V_{TH}$  because of body effect as source and bulk are not connected to each other so we will have voltage  $V_{sb}$  between them which increase value of  $V_{TH}$ .

7)  $g_m \gg g_{ds}$  .

8)  $g_m > g_{mb}$  .

9)  $C_{gs} > C_{gd}$  .

10)  $C_{sb} > C_{db}$  .

## 2. AC Analysis

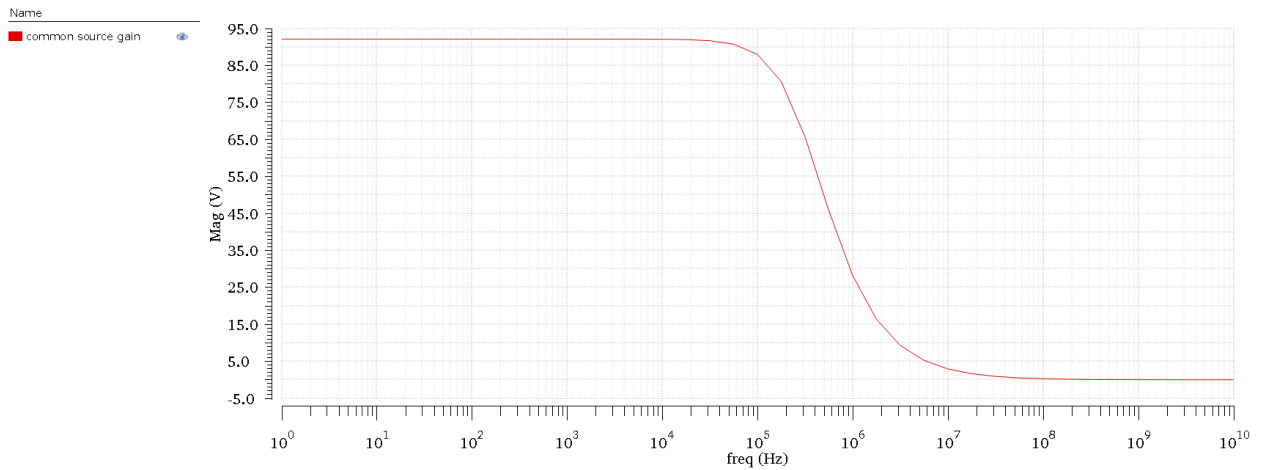


Figure 7 common source gain versus frequency

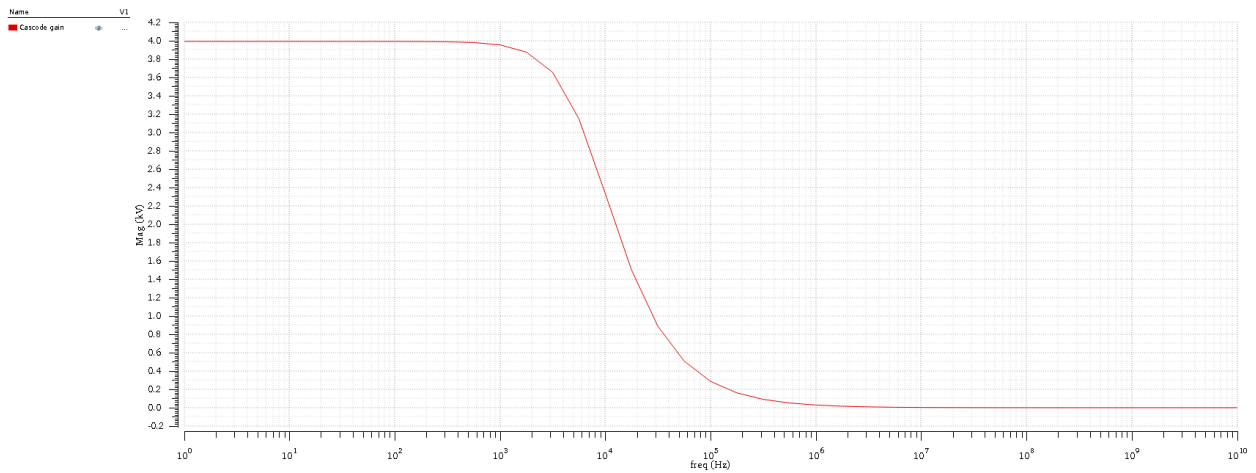


Figure 8 cascode amplifier gain versus frequency

• from simulation we found:

$$A_{vcs} = 92.13$$

$$A_{vcascode} = 3.993k$$

Comment: cascode amplifier gain is greater than common source amplifier gain .

- parameters from simulation ADEXL:




| Test            | Output                | Nominal   | Spec | Weight | Pass/Fail |
|-----------------|-----------------------|---|------|--------|-----------|
| LAB03:Cascode:1 | common source gain    |  |      |        |           |
| LAB03:Cascode:1 | dB20(VF("/Vout1"))    |  |      |        |           |
| LAB03:Cascode:1 | dc gain               | 92.13   |      |        |           |
| LAB03:Cascode:1 | dc gain in dB         | 39.29   |      |        |           |
| LAB03:Cascode:1 | cs bandwidth          | 323k  |      |        |           |
| LAB03:Cascode:1 | cs gbw                | 29.85M  |      |        |           |
| LAB03:Cascode:1 | cs ugf                | 30.47M  |      |        |           |
| LAB03:Cascode:1 | cascode gain in dB    |  |      |        |           |
| LAB03:Cascode:1 | cascode dc gain       | 3.993k  |      |        |           |
| LAB03:Cascode:1 | cascode dc gain in dB | 72.03   |      |        |           |
| LAB03:Cascode:1 | cascode bandwidth     | 7.35k   |      |        |           |
| LAB03:Cascode:1 | cascode gbw           | 29.42M  |      |        |           |
| LAB03:Cascode:1 | cascode ugf           | 29.86M  |      |        |           |

Figure 9 results of parameters from simulation

#### RESULTS from ADEXL:

|            | Common source | Cascode amplifier |
|------------|---------------|-------------------|
| Gain       | 92.13         | 3.993K            |
| Gain in dB | 39.29         | 72.03             |
| BW         | 323K          | 7.35K             |
| GBW        | 29.85K        | 29.42M            |
| UGF        | 30.47M        | 29.86M            |

- Bode plot of common source amplifiers in dB:

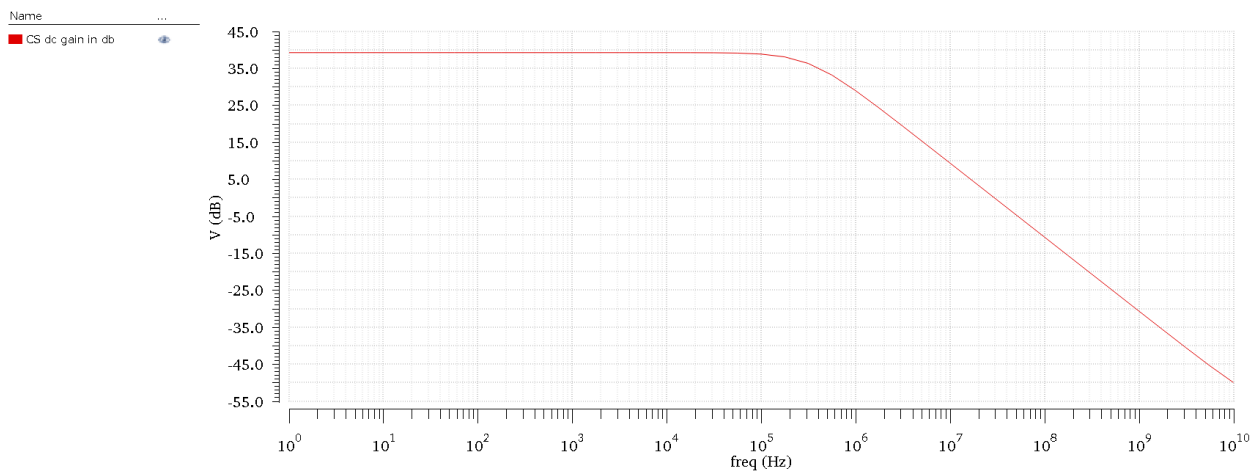


Figure 10 Bode plot of cs ib dB

- Bode plot of cascode amplifiers in dB:

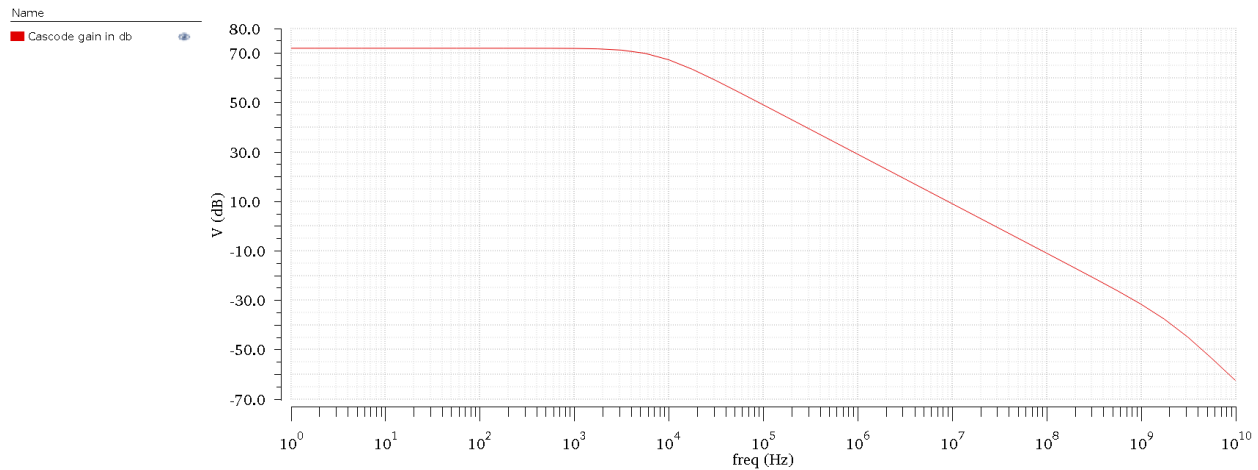


Figure 11 Bode plot of cascode in Db

Hand analysis:

$$|A_{VCS}| = g_{m1} * r_o = g_{m1} * \frac{1}{g_{ds}} = 187.3\mu * \frac{1}{2.033\mu} = 92.129$$

$$|A_{VCascode}| = g_{m1} * (r_{o1} + r_{o2} + (g_{m2} + g_{mb2}) * r_{o1} * r_{o2})$$

$$= 184.4\mu * \left( \frac{1}{3.926\mu} + \frac{1}{2.797\mu} + (188.3\mu + 46.69\mu) * \frac{1}{3.926\mu} * \frac{1}{2.797\mu} \right) = 4.059K$$

$$BW_{CS} = \frac{1}{2\pi * R * C} = \frac{1}{2\pi * \frac{1}{2.033\mu} * 10^{-12}} = 323.562KHZ$$

$$BW_{Cascode} = \frac{1}{2\pi * R * C} = \frac{1}{2\pi * 22.012 * 10^{-12}} = 7.23HZ$$

$$GBW_{CS} = BW_{CS} * Gain_{CS} = 9.129 * 323.562K = 29.81MHZ$$

$$GBW_{Cascode} = BW_{cascode} * Gain_{Cascode} = 7.23 * 4.059K = 29.347MHZ$$

Comment:

As shown in previous results The cascode amplifier has a higher gain than the common source amplifier because the common base transistor in the cascode amplifier effectively multiplies the output resistance of the common source transistor. This is because the common base transistor has a very high output resistance, which is not affected by the input voltage because of higher resistance of cascode amplifier than common source, cascode has lower bandwidth as bandwidth